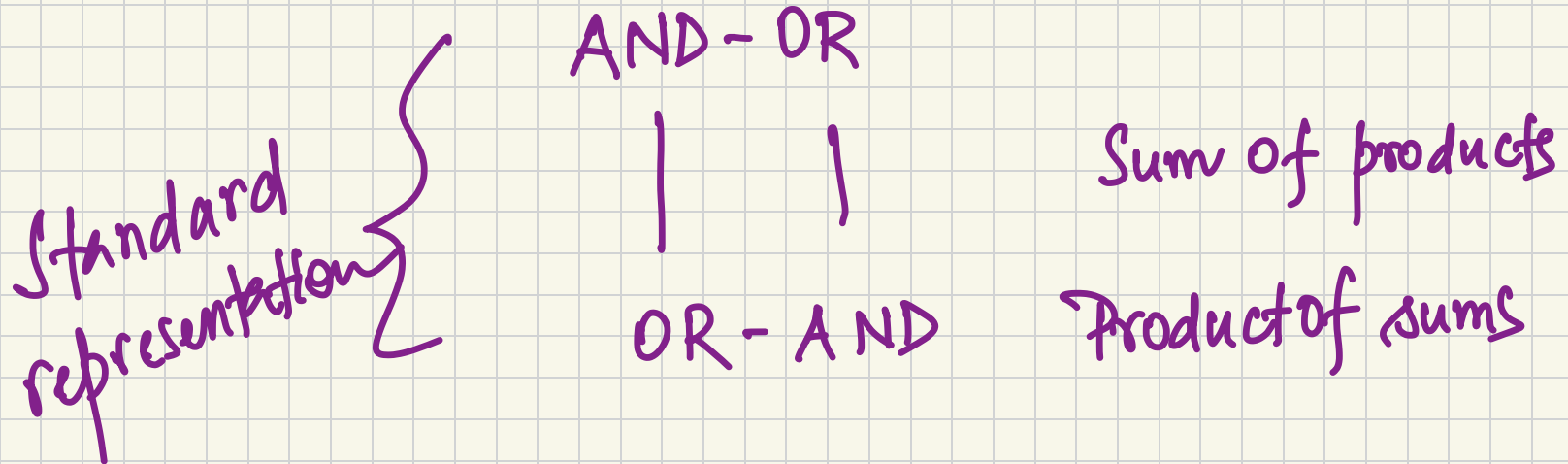


ACOL 215

(29th Sept.)

Two-level implementations

AND, OR, NAND, NOR gates




Some combinations are degenerate.

AND - AND

OR - OR

NOR - NAND (OR)

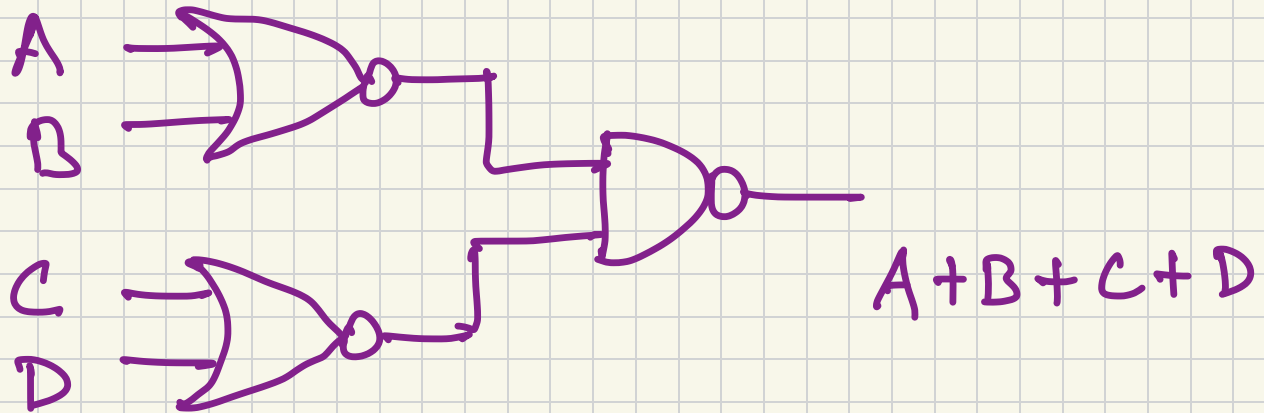

What about NAND-NOR?
(AND)

The non-degenerate forms are :


AND - OR
NAND - NAND

OR - AND
NOR - NOR


seen
already

NOR - OR
OR - NAND

NAND - AND
AND - NOR

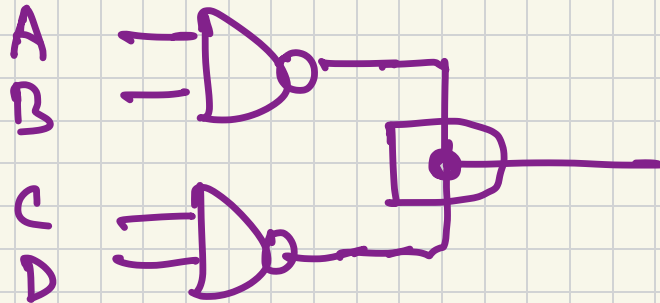


$$F = (AB + CD)'$$

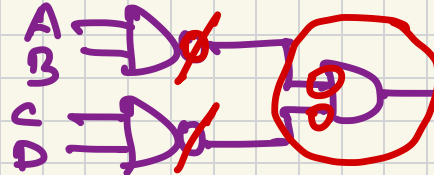

NOR gate
in invert-AND
graphical representation

NOR-OR

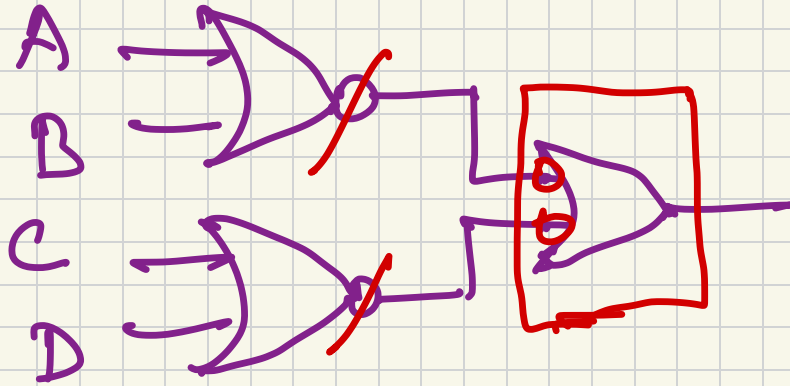

$$F = ((A+B)(C+D))'$$

NAND gate in
invert-OR graphical
representation

OR-AND-Invert function

Exercise Implement the following function with


- i) AND-NOR gates ii) NAND-AND gates
- iii) OR-NAND gates iv) NOR-OR gates

$z + xy' + x'y$

	yz 00	01	11	10
x 0	m_0 1	m_1 0	m_3 0	m_2 0
1	m_4 0	m_5 0	m_7 0	m_6 1


$F = x'y'z' + xy'z'$
 $F' = (x'y'z' + xy'z')$
 $= (x+y+z)(x'+y'+z)$
 $F = ((x+y+z)(x'+y'+z))'$

$$((x+y+2)(x'+y'+2))'$$

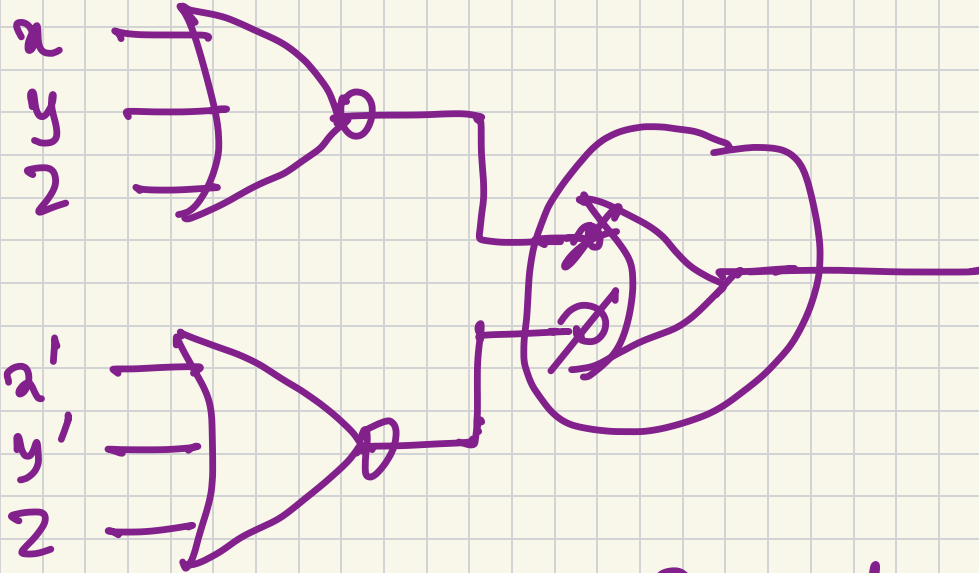

$$f = (xy' + x'y + 2)'$$

$$(xy' + x'y + z)'$$

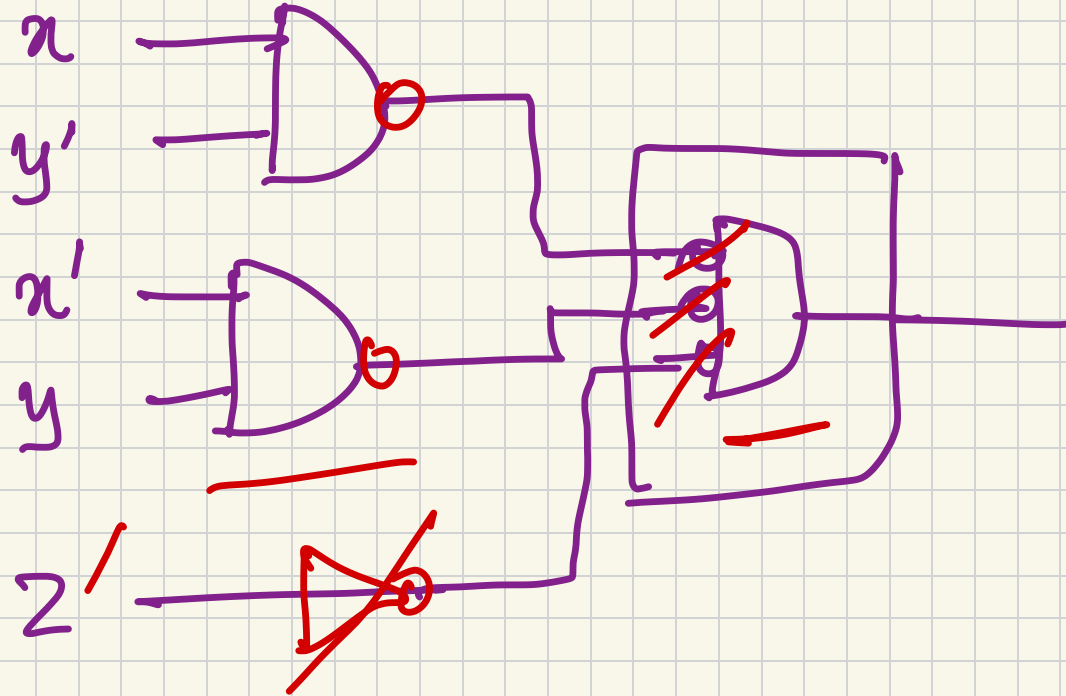


XOR gates (Exclusive -OR gates) \oplus

$$x \oplus y = xy' + x'y$$

Exclusive -NOR (XNOR)

$$(x \oplus y)' = xy + x'y'$$

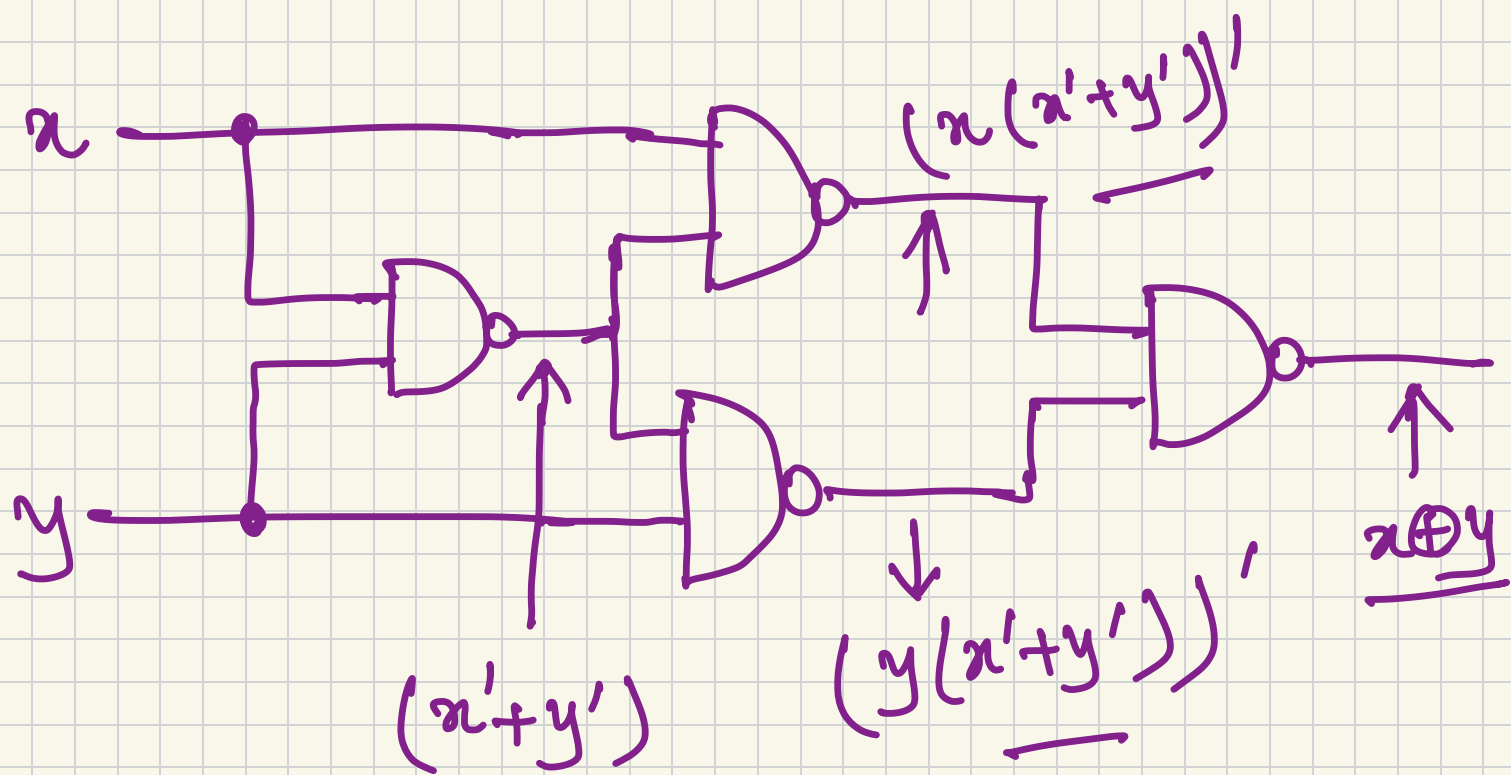

$$\begin{aligned}
 & x(x'+y') + y(x'+y') \\
 &= xx' + xy' + yx' + yy' = xy' + x'y
 \end{aligned}$$

$$x \oplus y$$

		y ₂			
		00	01	11	10
x ₂	0	m ₀ ↓	m ₁ ↓	m ₃ ↓	m ₂ ↓
	1	m ₄ ↓	m ₅ ↓	m ₇ ↓	m ₆ ↓

even

$$\underline{x \oplus y \oplus z}$$


can be extended to
multiple inputs
(both commutative and
associative)

$$\underline{x \oplus y \oplus z}$$

odd

$$= \underline{(xy' + x'y)z'} + \underline{(xy' + x'y)'z}$$
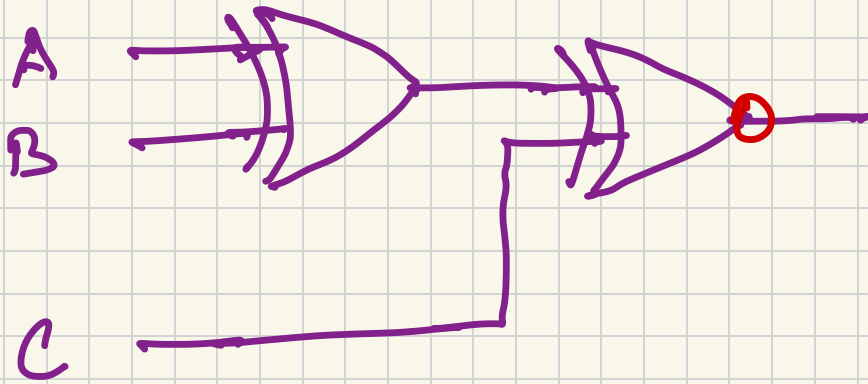
$$= \underline{xy'z' + x'yz' + xy z + x'y'z}$$



3-input odd function
even

Parity generation and checking

XOR functions are useful in systems requiring error detection and correction.

A parity bit is an extra bit included with a binary string (message) to make the number of 1's either even or odd.

Even parity bit generator (for a 3-bit message)

x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = x \oplus y \oplus z$$


Parity checker

$x \ y \ z \ P$
~~~~~  
even no. of 1's

~~~~~  
odd no. of 1's

$\underline{\underline{C}}$
 $\underline{0}$ (no error)
 1 (error)
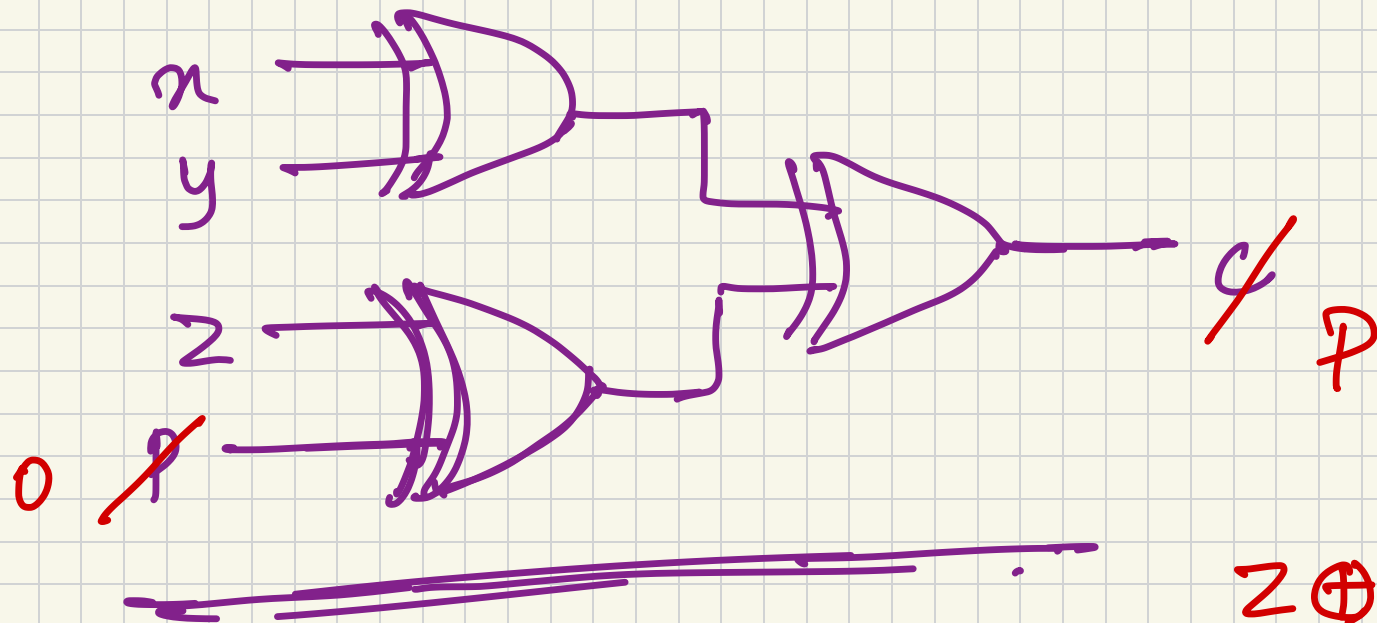
$$C = \underline{x \oplus y \oplus z \oplus P}$$



$$z \oplus 0 = z$$

Chapter 4 \updownarrow
Exercise
Combinational and Sequential \parallel
Circuits \parallel
 Read sect. 3.9 and 3.10 \updownarrow
 HDL \updownarrow
 storage element $\}$