 


Multiplexers

ACOL215

(28th Oct.)

Combinational circuits that select binary information from one of many input lines and directs it to a single line.



when $S = 0$


output = I_0

when $S = 1$

output = I_1


Two-to-one line multiplexer

Four-to-one line multiplexer

 

S_1	S_0	output
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Block diagram

 


A multiplexer
is also called
a data-selector.

The AND gates (and the inverter
gates) "decode" the selection
input lines.

A 2^n -to-1 line multiplexer is constructed from an n -to- 2^n line decoder by adding 2^n input lines to it (one line to each AND gate) and the outputs of the AND gates are applied to a single OR gate.

Like in decoders, multiplexers can also have an enable input to control its operation.


(Example on next slide)

 

Implement Boolean Functions with Multiplexers

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F	
0	0	0	0	z
0	0	1	1	
0	1	0	1	z'
0	1	1	0	
1	0	0	0	0
1	0	1	0	
1	1	0	1	1
1	1	1	1	

 


4x1 multiplexer

F

S_1	S_0	
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$F(A, B, C, D) =$$

$$\sum(1, 3, 4, 11, 12, 13, 14, 15)$$

 

A	B	C	D	E	
0	0	0	0	0	A
0	0	0	1	1	
0	0	1	0	0	A
0	0	1	1	1	
0	1	0	0	1	A'
0	1	0	1	0	
0	1	1	0	0	0
0	1	1	1	0	
1	0	0	0	0	0
1	0	0	1	0	
1	0	1	0	1	A
1	0	1	1	1	
1	1	0	0	1	1
1	1	0	1	1	
1	1	1	0	1	1
1	1	1	1	1	

Exercise

Implement

$$F(A, B, C) = \sum (3, 5, 6, 7)$$

with a multiplexer.

Reading Exercise

Three-state gates

(Page No. 204 in the book)

Next class

Synchronous Sequential
Logic
(chapter 5)