

ACOL215

(26th Nov.)

Ring counter


Timing signals

↳ control the sequence of operations in a digital system

↳ can be generated using a shift register
(or by a counter using a decoder).

A ring counter is a circular shift register with only one flip-flop being set at any particular time.

 
→ And this single bit is shifted from one flip-flop to the next to produce the timing signals.




Initialised to 1000

t_3
 t_2
 t_1
 t_0

1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

 

 An alternate design is to use a two bit counter that goes through four distinct states and then use a 2-to-4-line decoder.



In general, to generate 2^n timing signals, we need either a shift register with 2^n flip-flops, or an n -bit counter with n -to- 2^n -line decoder.

16 flip-flops

4 flip-flop
+ 16 AND-gates
(4-input AND gate)


Johnson's counter

- uses fewer than 2^n flip-flops
- decodes only using two-input AND-gates.

Idea

A K -bit ring counter circulates a single bit among the flip-flops to provide K distinguishable states.

 this number can be doubled if
the shift register is connected
as a switch-tail ring counter.



$$D_C = (A + C)B$$

Flip flop outputs

A	B	C	E
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1

AND-gate required for output

$A'E'$

AB'

BC'

CE'

AE

$A'B$

$B'C$

$C'E$

