

ACOL215


(Oct. 7<sup>th</sup>)


## Binary Subtractor

$$A - B$$

add:  $A$ , 2's complement of  $B$

$A$ , 1's complement of  $B$ , 1

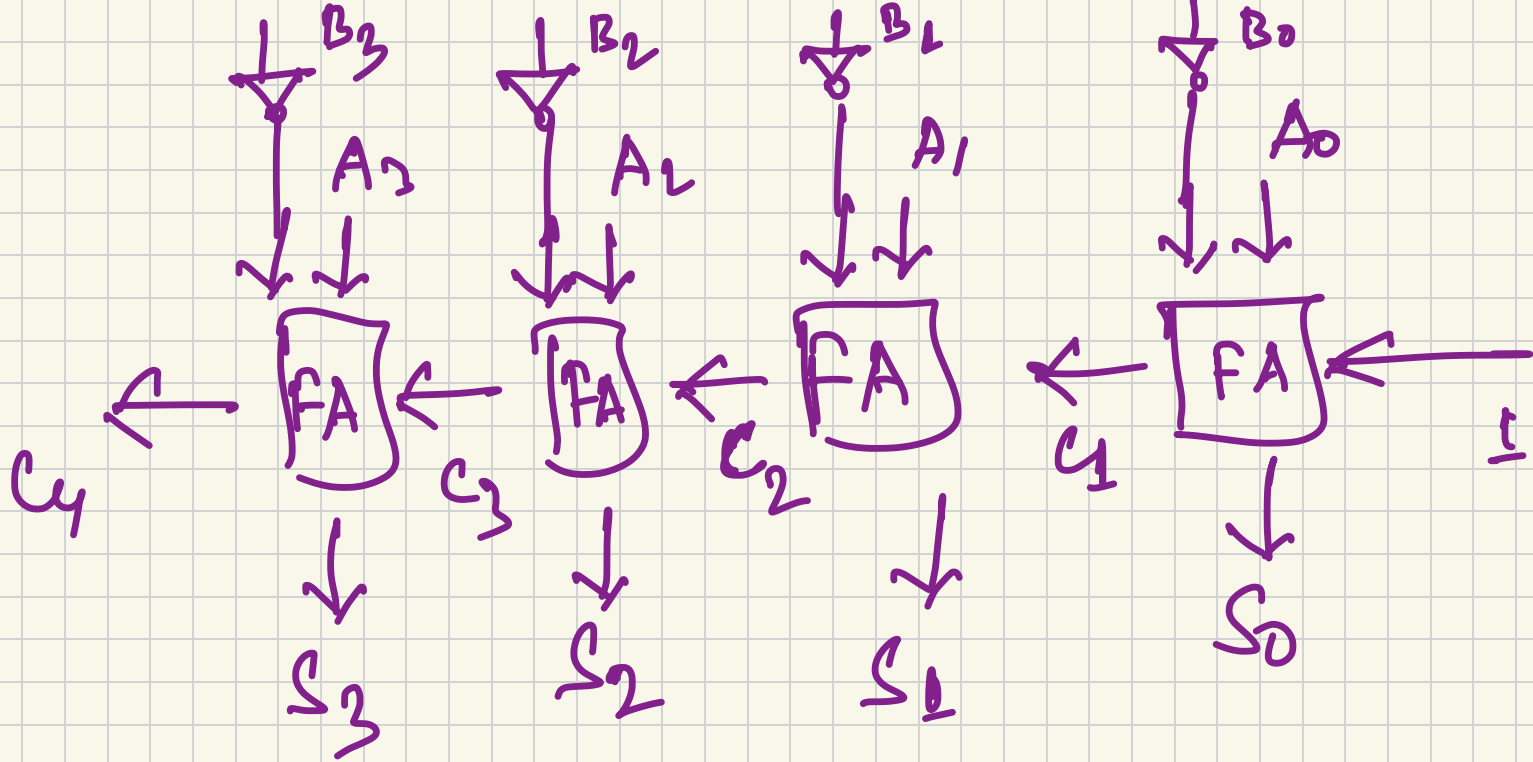

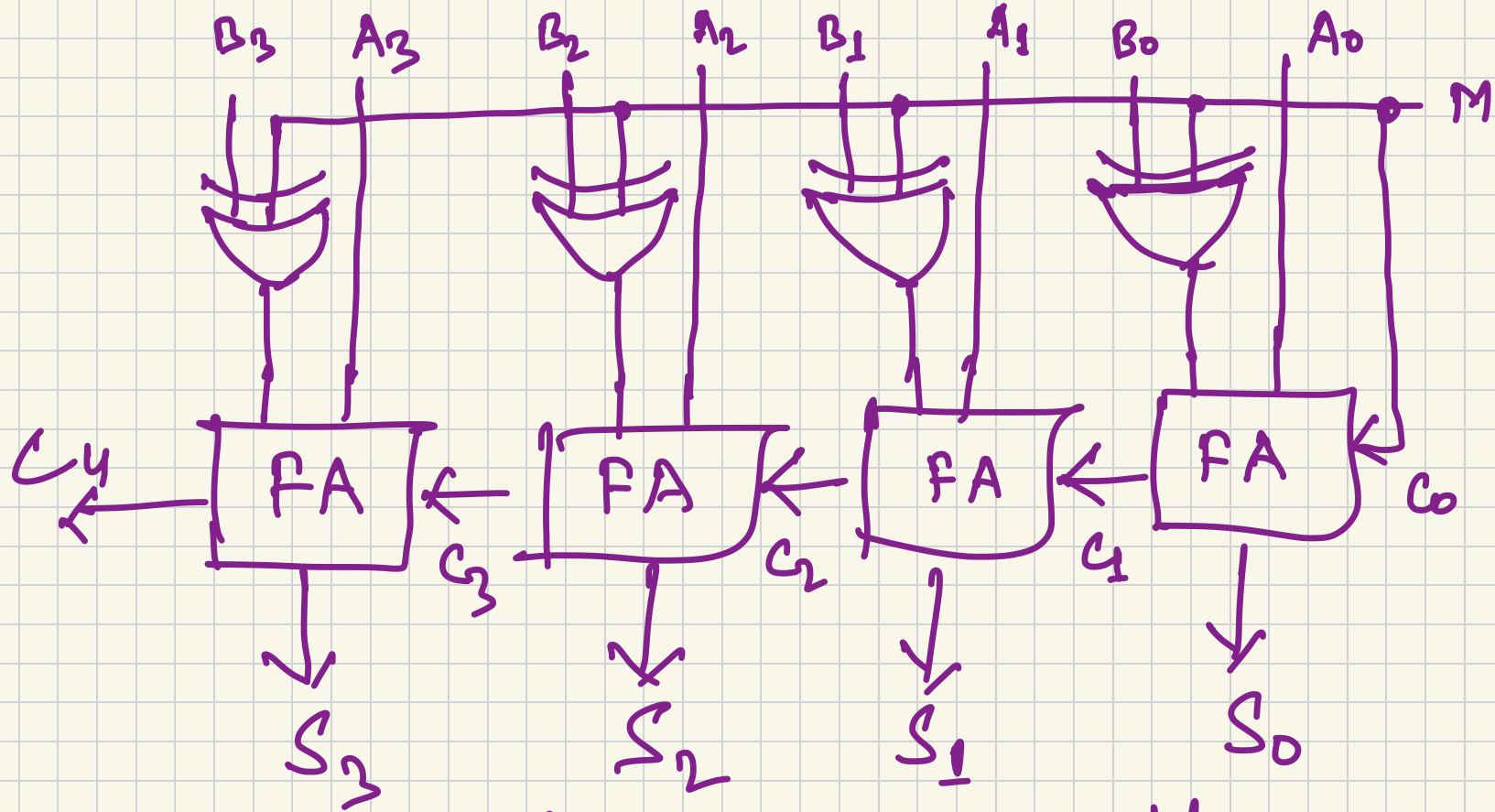

If

$M = 0$

$M = 1$

← adder  
← subtractor

# Overflow

When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant digit.

For signed numbers

→ left most bit represents the sign

→ negative numbers are in 2's complement form.

When two signed numbers are added, the sign bit is treated as a part of the number and the end carry does not indicate an overflow.

Note that an overflow cannot occur after an addition if one number is positive and the other is negative.

Consider

$\boxed{0!} \rightarrow \text{last two carries} \leftarrow \boxed{10}!!$

$$+70 \quad 01000110$$

$$+80 \quad 01010000$$

---

$$10010110$$

↑  
a negative number!


$$-70 \quad 10111010$$

$$-80 \quad 10110000$$

---

$$01101010$$

↑  
a positive number!

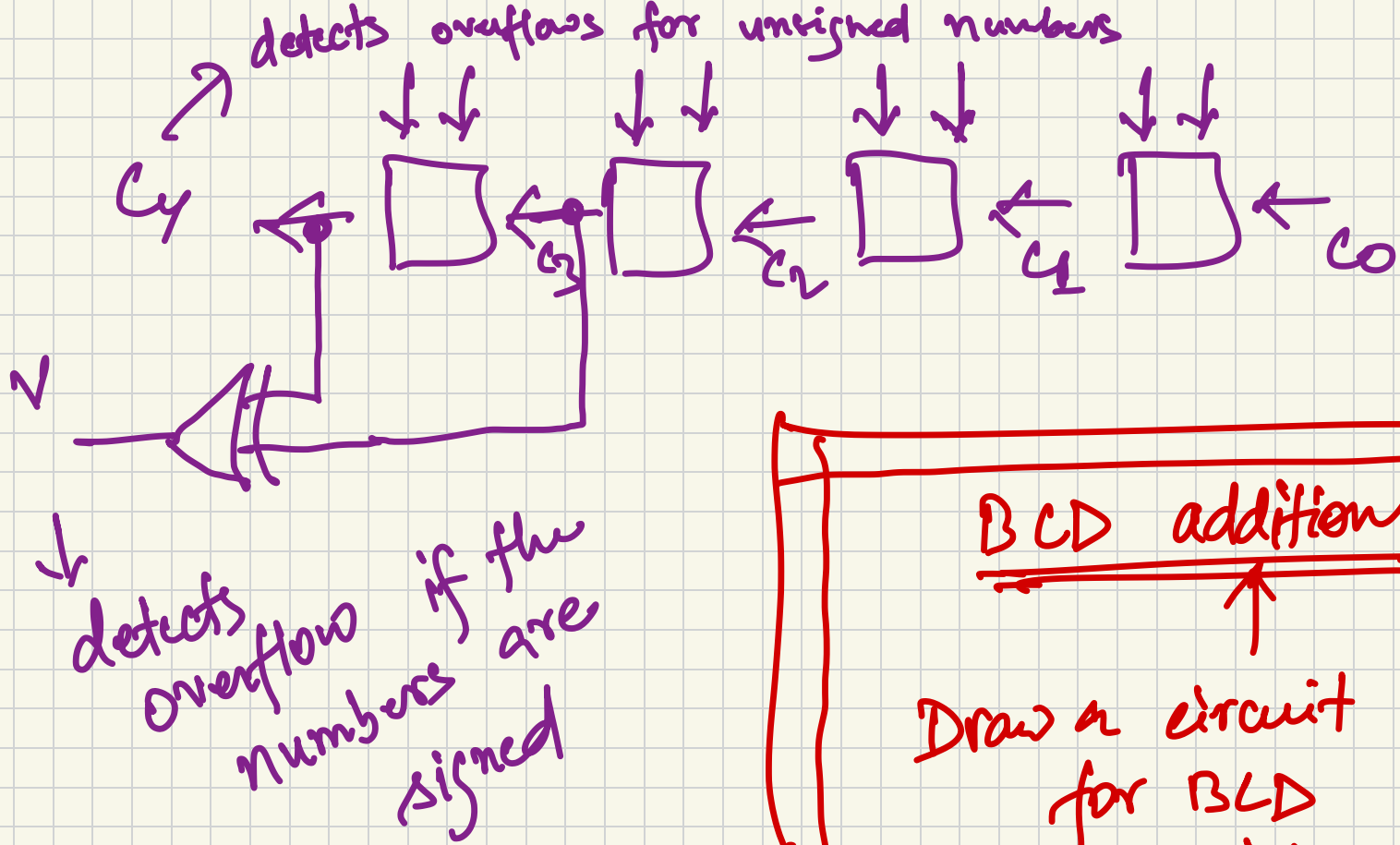

BCD addition (sect. 1.7)

Draw a circuit for BCD addition.  
chapter 4

# Binary Multiplication

$B_1$   $B_0$

$A_1$   $A_0$

---

$A_0B_1$   $A_0B_0$


$A_1B_1$   $A_1B_0$

---

$A_1B_1$   $A_0B_1 + A_1B_0$   $A_0B_0$

---

$P_3$   $P_2$   $P_1$   $P_0$

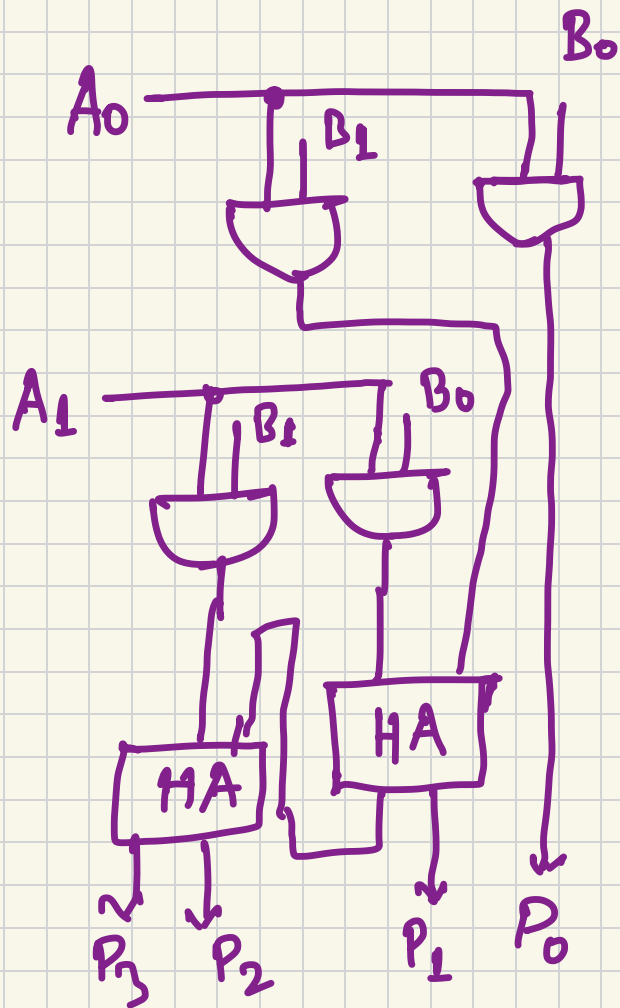




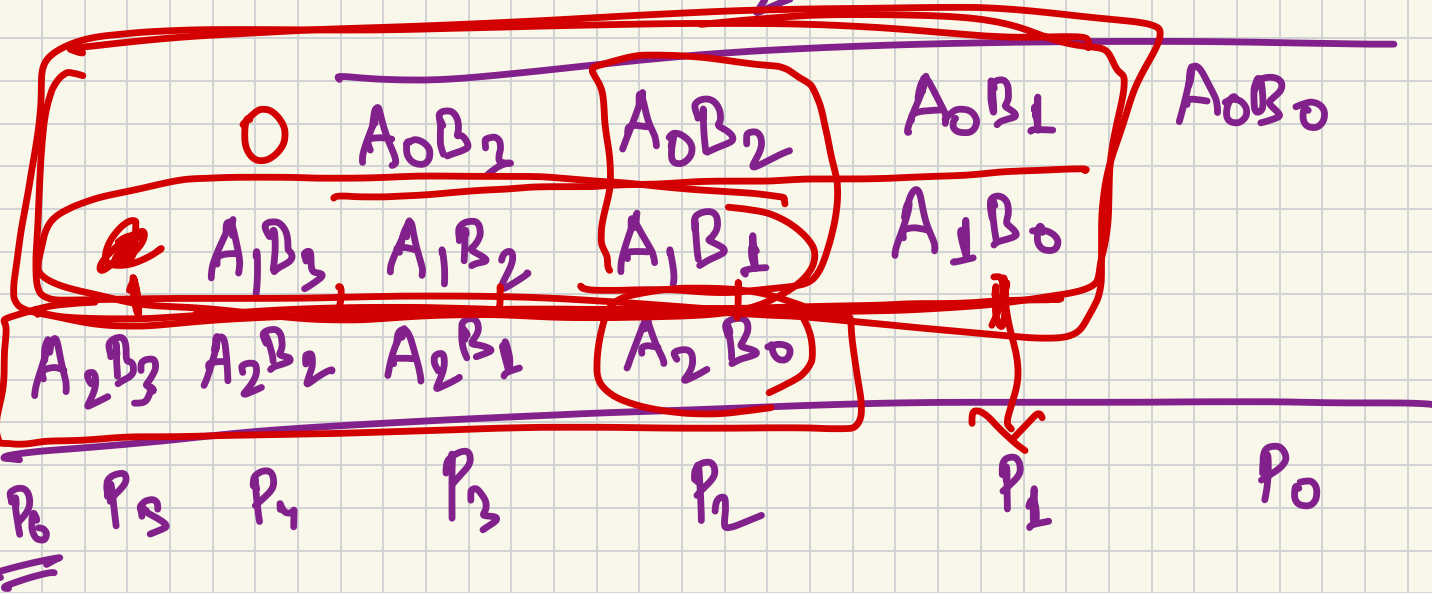
# Exercise

Draw the multiplier circuit for

$B_3 \quad B_2 \quad B_1 \quad B_0$   
 $A_2 \quad A_1 \quad A_0$



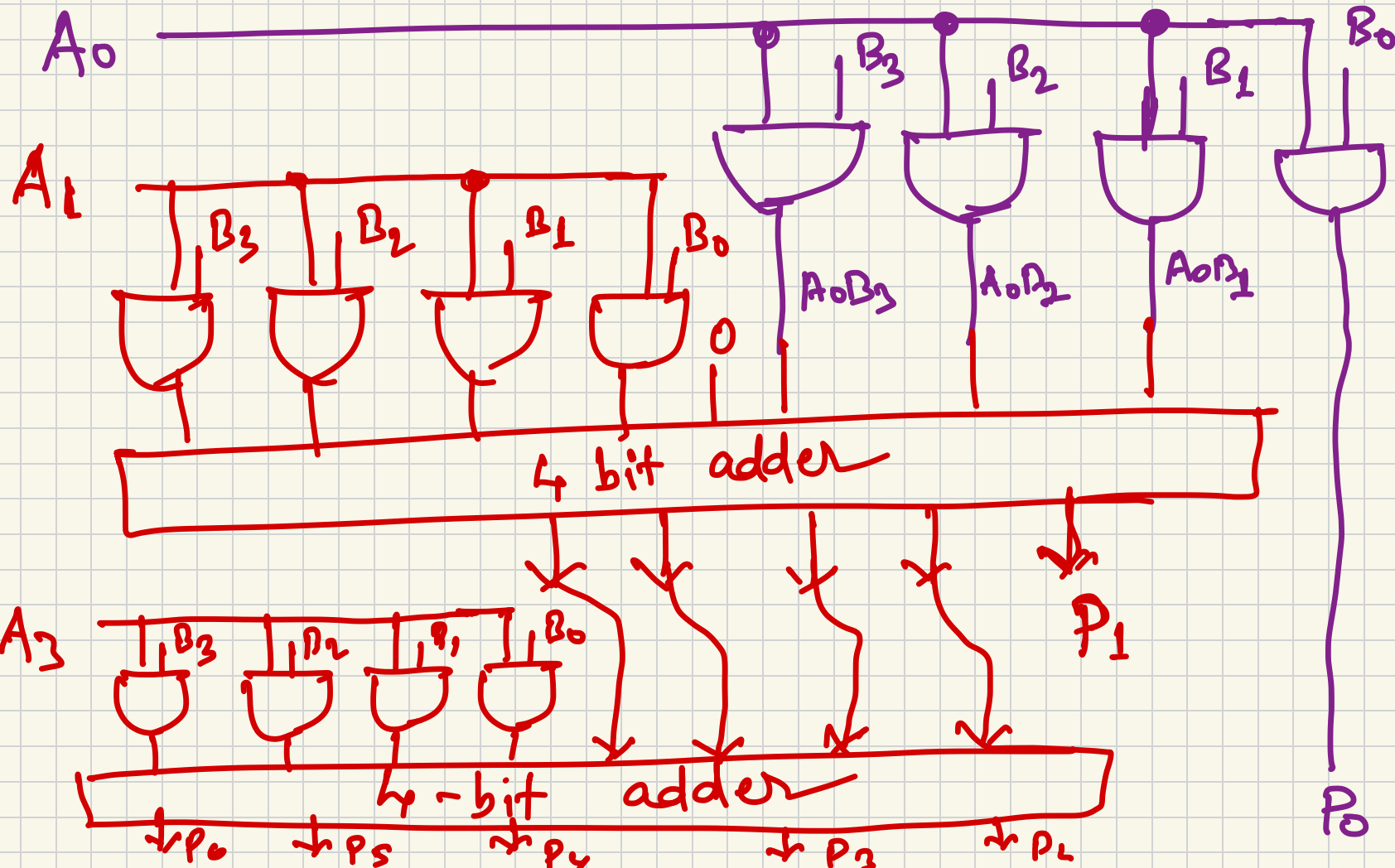

# Magnitude Comparator

$$\frac{A}{n} \quad \frac{B}{n}$$

$$A = B \quad / \quad A > B \quad / \quad A < B$$

$$\frac{A = B}{\underline{\underline{\quad}}}$$

$$\begin{array}{cccc} A_3 & A_2 & A_1 & A_0 \\ B_3 & B_2 & B_1 & B_0 \end{array}$$

$$\frac{A_3 = B_3}{\underline{\quad}} \quad \text{and} \quad \frac{A_2 = B_2}{\underline{\quad}} \quad \text{and} \quad \frac{A_1 = B_1}{\underline{\quad}} \quad \text{and} \quad \frac{A_0 = B_0}{\underline{\quad}}$$

$$x_i = \frac{A_i B_i}{(A = B)} + \frac{A_i' B_i'}{x_3 x_2 x_1 x_0}$$

$$A > B$$

$$A_3 B_3' + \alpha_3 A_2 B_2' + \alpha_3 \alpha_2 A_1 B_1' + \alpha_3 \alpha_2 \alpha_1 A_0 B_0'$$



$$A < B$$

$$A_3' B_3 + \alpha_3 A_2' B_2 + \alpha_3 \alpha_2 A_1' B_1 + \alpha_3 \alpha_2 \alpha_1 A_0' B_0$$

## Exercise

Draw the circuit for a  
4-bit magnitude  
comparator.

A's and B's

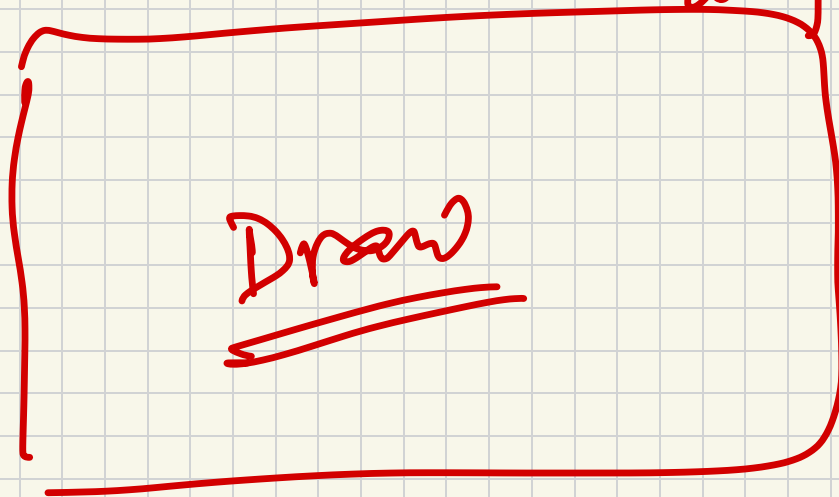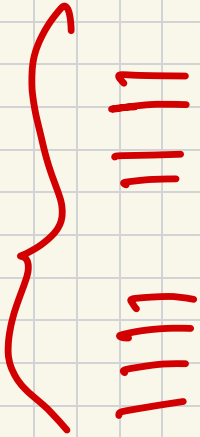

- $(A=B)$
- $(A>B)$
- $(A<B)$

Output

Next lecture : Decoders, Encoders, Multiplexers