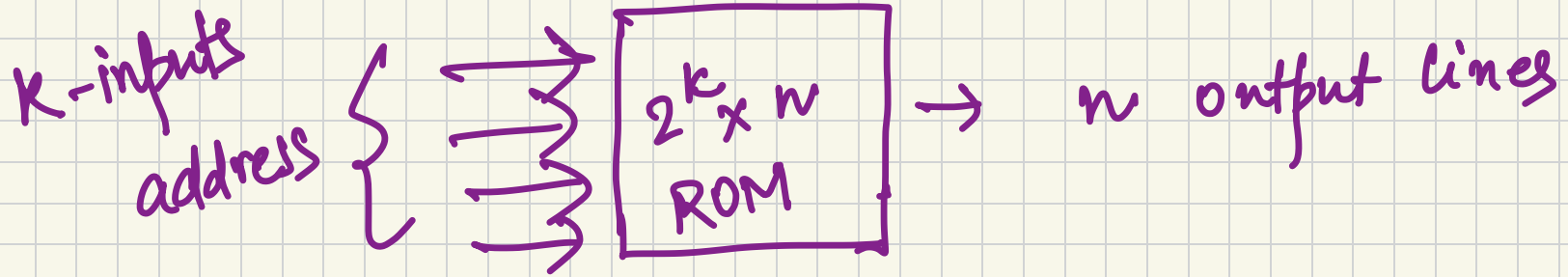



ACOL215

(9th Dec.)

Read Only Memory (ROM)



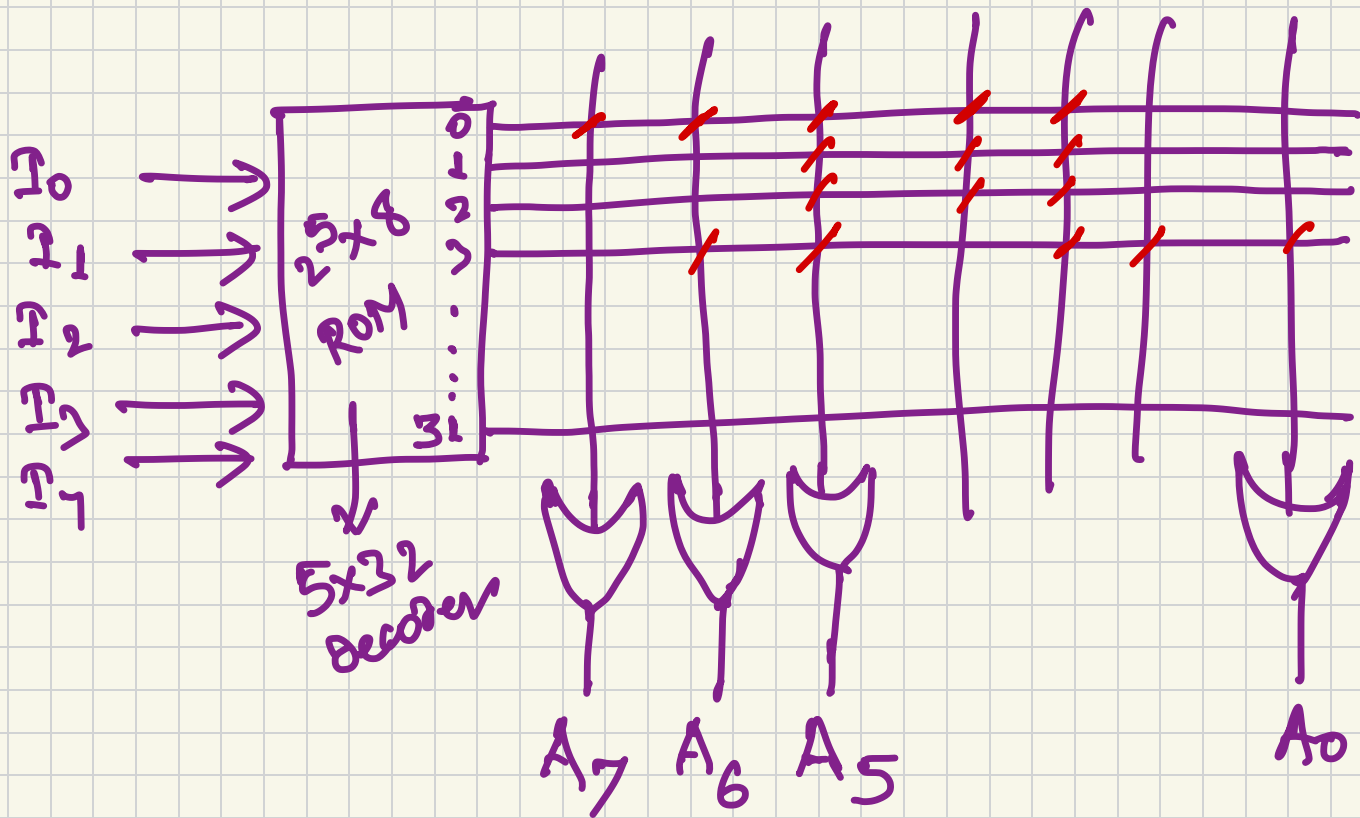↓
 $2^5 \times 8$ ROM
 32×8 ROM } next slide



256 intersecting
crosspoints

↓
These intersections
are programmable.

A programmable connection is like
a switch that can be altered to
be in a closed state
(the lines are connected)
or an open state
(the lines are disconnected)


The internal storage of
a ROM can be specified by
a truth table

Inputs

I_4	I_3	I_2	I_1	I_0
0	0	0	0	0
0	0	0	0	1
0	0	0	1	0
0	0	0	1	1
.				
1	1	1	1	0
1	1	1	1	1

Outputs

A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
1	0	1	0	0	1	1	0
0	1	1	1	1	0	0	0
1	0	0	0	1	1	1	0
.							
1	1	1	0	0	0	0	0
0	1	0	1	1	1	1	0

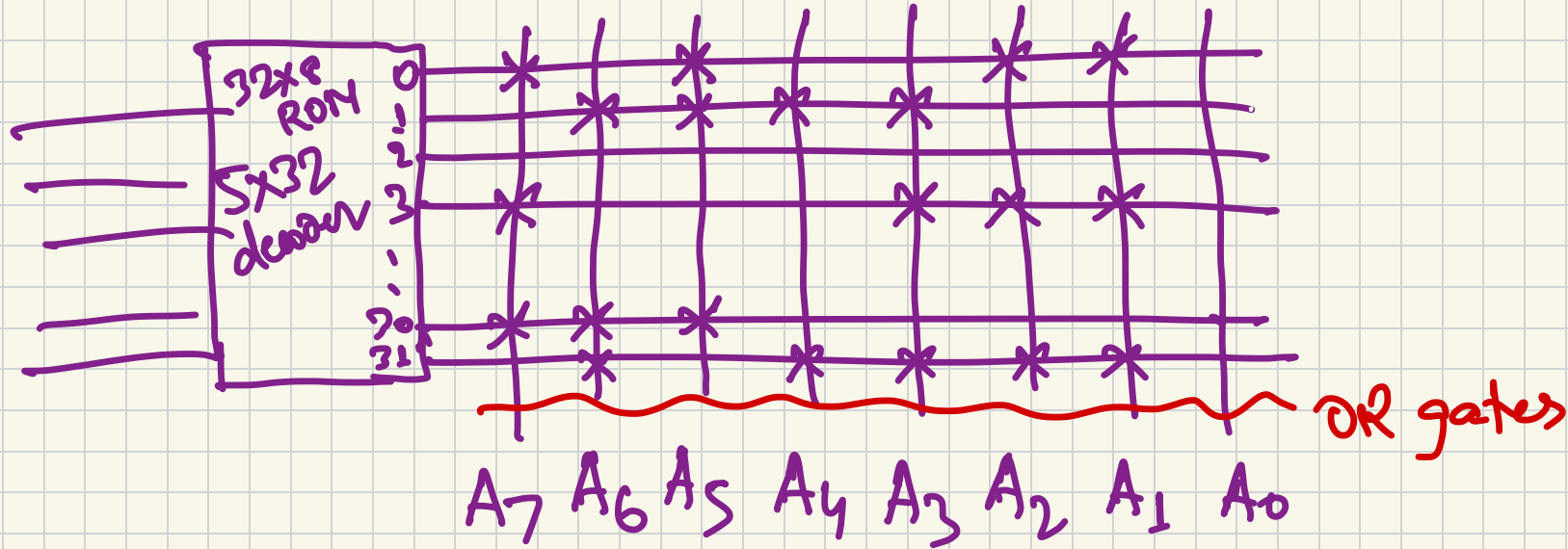

We can also consider each output terminal as a Boolean function expressed as a sum of minterms.

$$A_7(I_4, I_3, I_2, I_1, I_0) = \sum(0, 3, \dots, 30)$$

$$A_2(\dots) = \sum(0, 3, \dots, 31)$$

Exercise Design a combinational circuit using a ROM — the circuit accepts a three bit number and outputs a binary number that is equal to the square of the input.

A_2 A_1 A_0

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1

Square

0

1

4

9

16

25

36

49

B_5 B_4 B_3 B_2 B_1 B_0

0 0 0 0 0 0

0 0 0 0 0 1

0 0 0 1 0 0


0 0 1 0 0 1

0 1 0 0 0 0

0 1 1 0 0 1

1 0 0 1 0 0

1 1 0 0 0 1

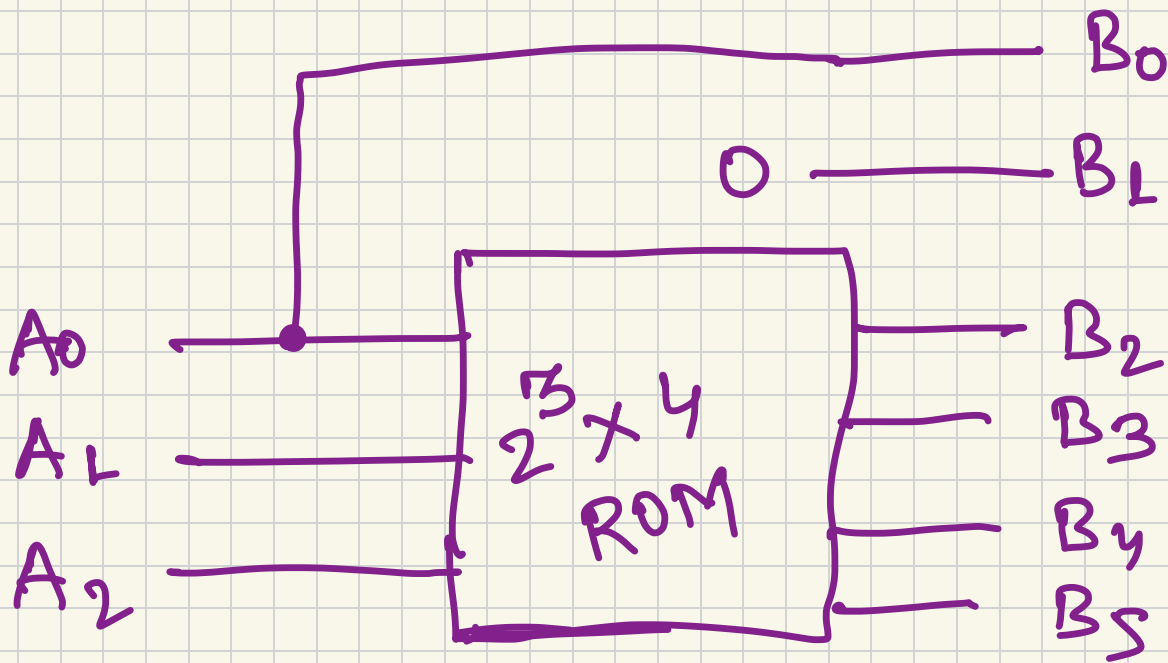

ROM truth table

A_2	A_1	A_0	B_5	B_4	B_3	B_2

Mask programming

→ during the fabrication process

PROM

Programmable ROM


- comes with all fuses intact
- "blow" some of them by applying high voltage
- once programmed, this is permanent

Erasable PROM


→ can be restructured to
the original state
by placing it under u/v
light

EEPROM

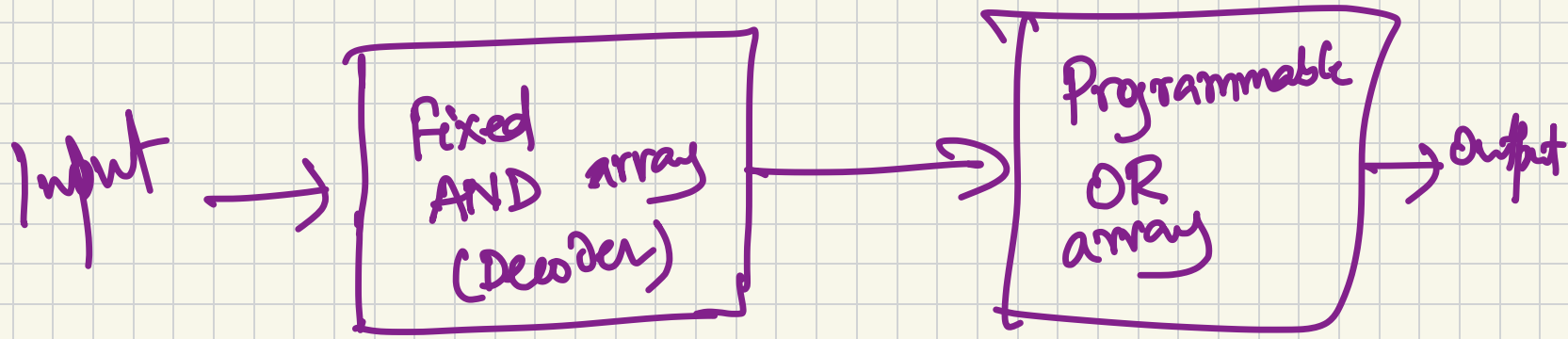↳ restructuring can be done
with electrical signals



(PROM) Programmable ROM

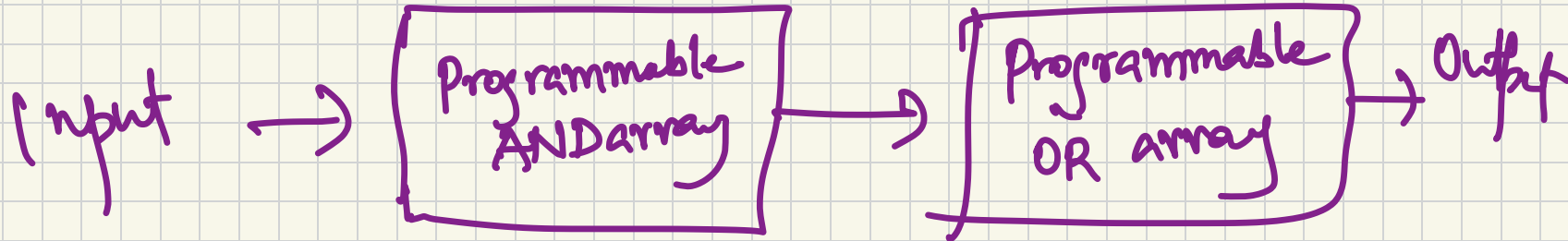

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

