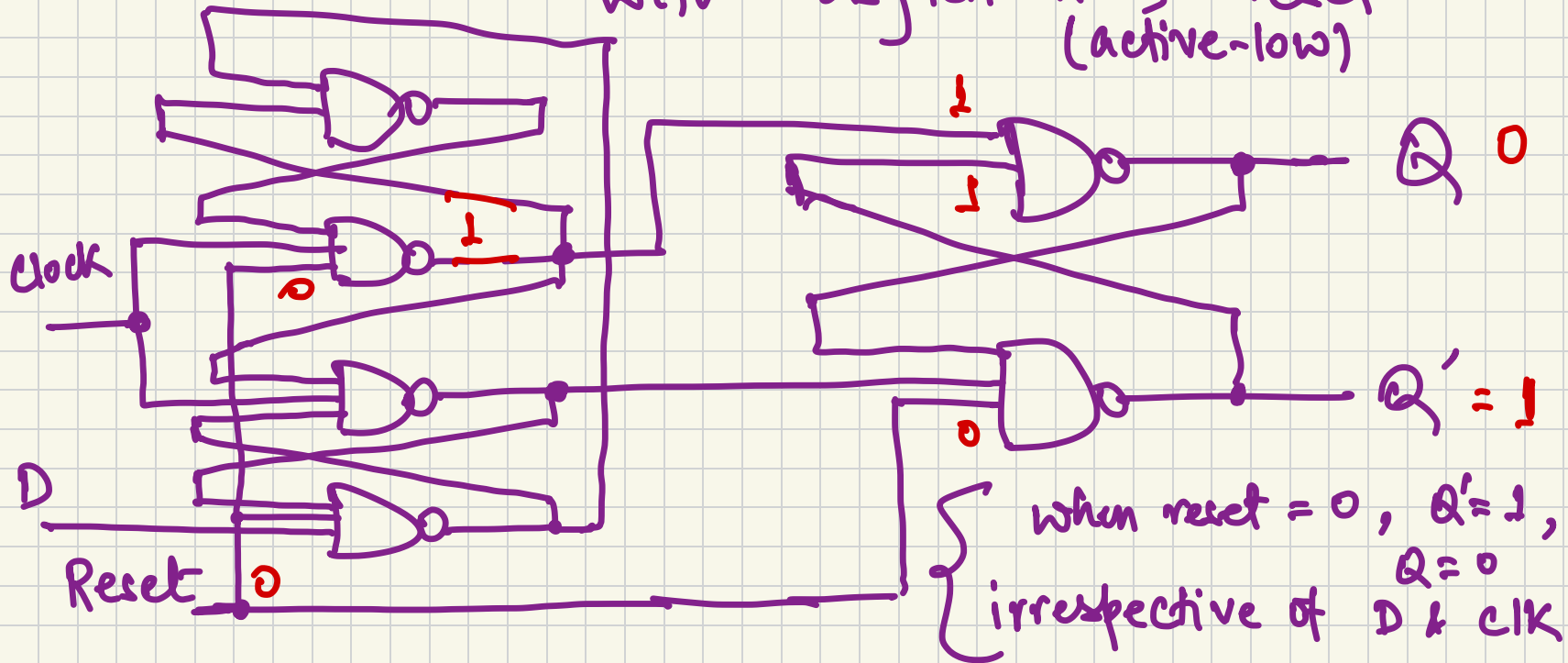


ACOL215

(10th Nov.)

Positive-edge triggered D flip-flop
with asynchronous reset
(active-low)



Exercise


asynchronous active-low set

set = 0 then $Q = 1$

When reset is 1 this
behaves like a positive
edge-triggered D flip-flop

Reset	clk	D	Q	Q'
1	↑	0	0	1
1	↑	1	1	0
0	x	x	0	1


Graphical symbol

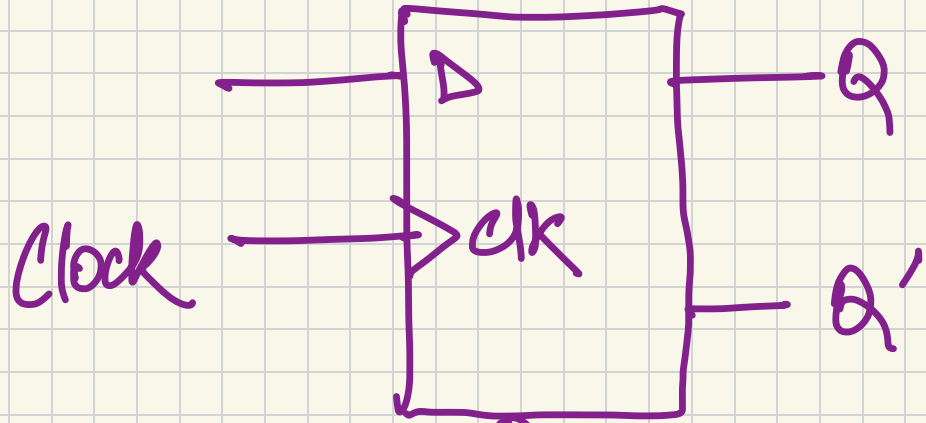

Reset

{ D Positive edge triggered flip-flop with active low reset

Analysis of clocked sequential circuits

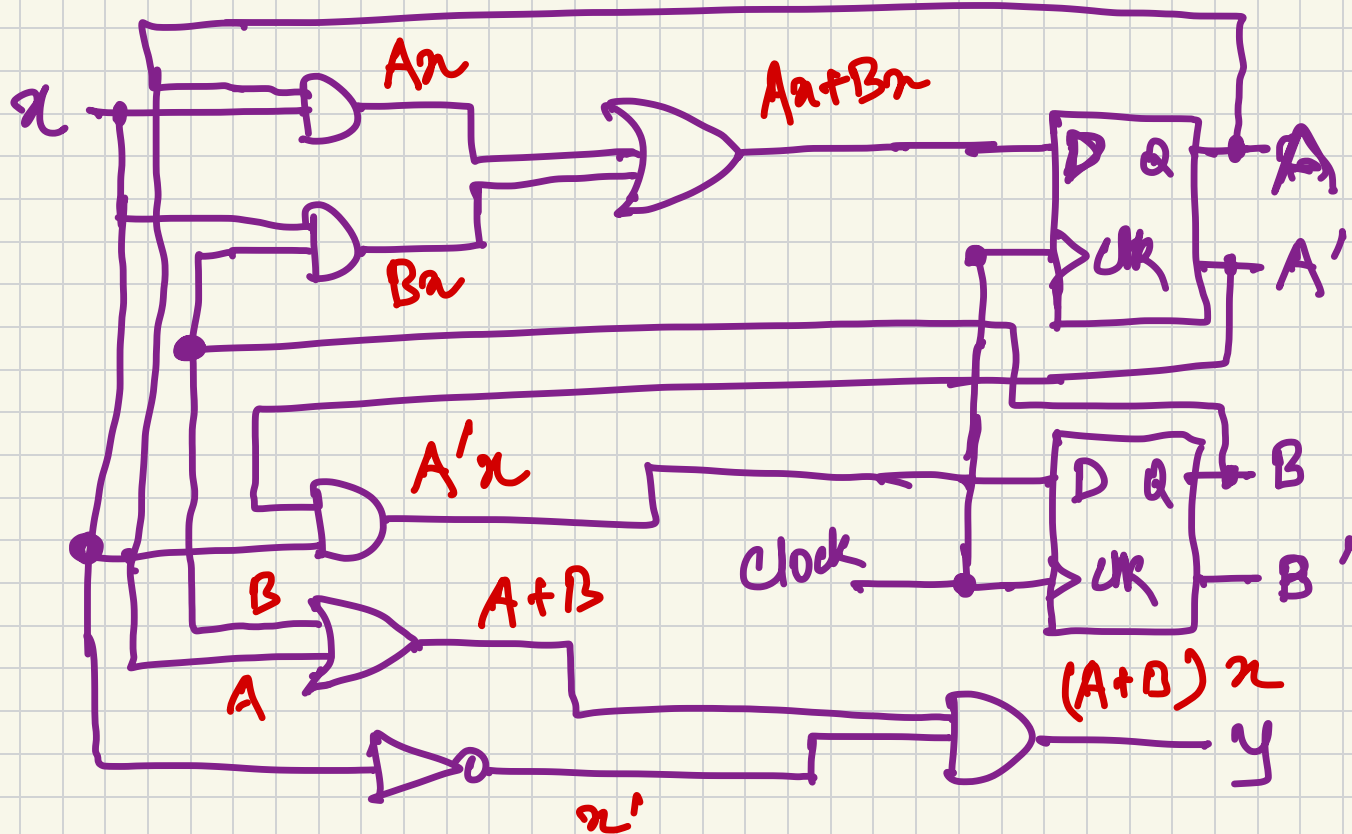

$$\textcircled{A(t+1)} = \frac{A(t)x(t) + B(t)x(t)}{Ax + Bx}$$

$$B(t+1) = \frac{A'(t)x(t)}{A'x}$$

$$y(t) = (A(t) + B(t))x'(t)$$

$$= (A + B)x'$$

$$= Ax' + Bx'$$

State table

Present state

A	B
0	0
0	0
0	1
0	1
1	0
1	0
1	1
1	1

Input

x
0
1
0
1
0
1
0
1


Next state

A	B
0	0
0	1
0	0
1	1
0	0
1	0
0	0
1	0

Output

y
0
0
1
0
1
0
1
0

State diagram

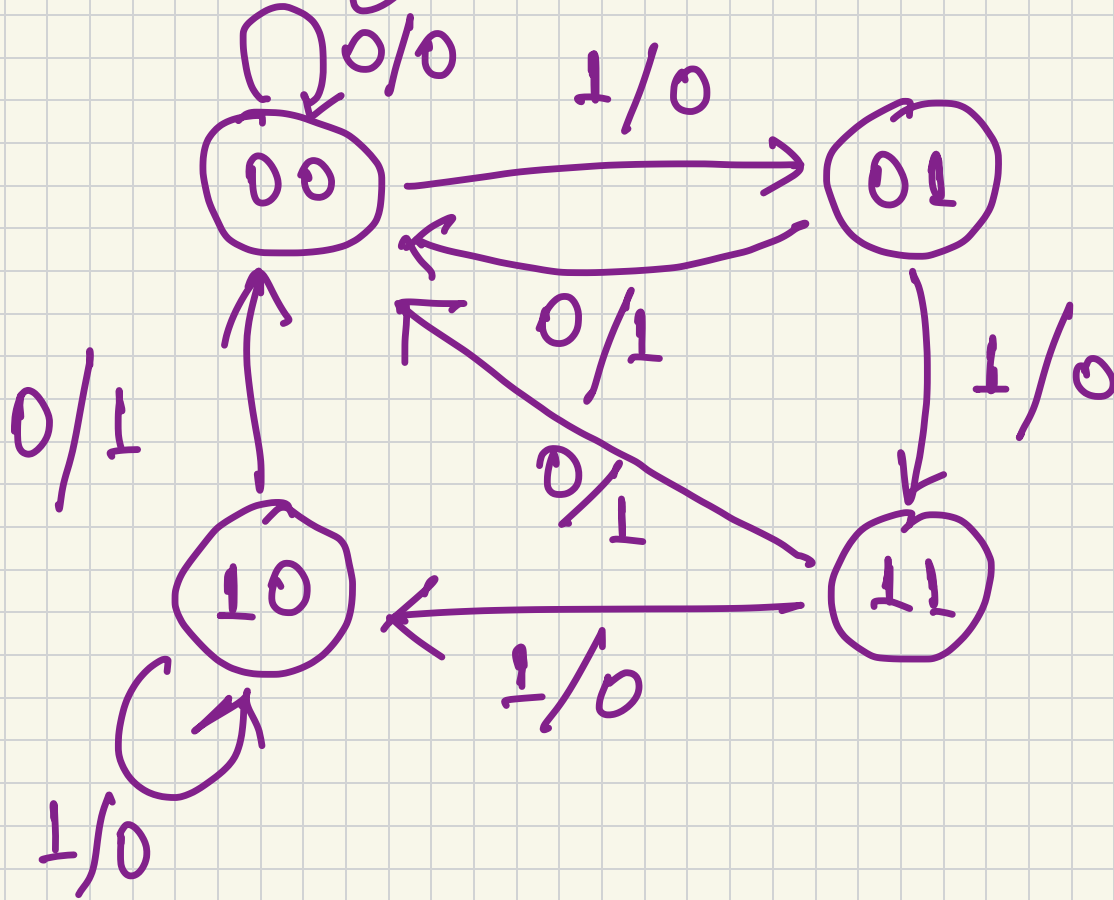

Alternate form (of the state table)

Present state		Next state		Output	
		$x=0$	$x=1$	$x=0$	$x=1$
A	B	A	B	y	y
0	0	0	0	0	0
0	1	0	0	1	0
1	0	0	0	1	0
1	1	0	0	1	0

Flip-flop input equations
(also called excitation equations)

flip-flop
input
eqns


$$D_A = Ax + Bx$$

$$D_B = A'x$$

$$y = (A+B)x'$$

} output
eqn

$$D_A = A \oplus x \oplus y$$

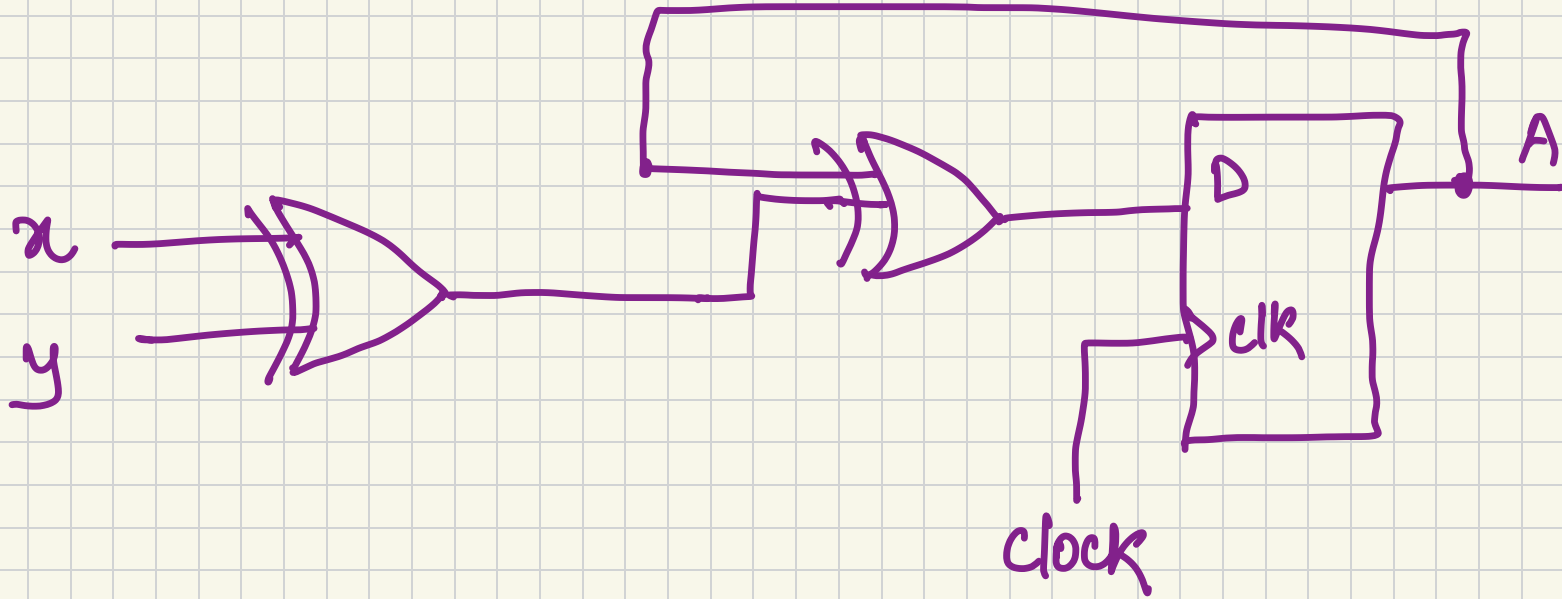

Present state

A

0

0

0

0

1

1

1

1

Inputs

x

y

0

0

0

1

1

0

1

1

0

0

0

1

1

0

1

1

Next state

A

0

1

1

0

1

0

0

1

