

ACOL 215

(Sept. 21st)

x y

0 0

0 1

1 0

1 1

x AND y

0

0

0

1

x OR y

0

1

1

1

x XOR y

(x OR y , but not both)

0

1

1

0

x y

0 0

0 1

1 0

1 1

NOR (NOT-OR)

($x \downarrow y$)

1

0

0

0

NAND (NOT-AND)

($x \uparrow y$)

1


1

1


0

$x \uparrow y$


x	y	F (constant function)	F'	Equivalence (NOT-XOR),
0	0	0	1	1
0	1	0	1	0
1	0	0	1	0
1	1	0	1	1

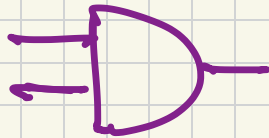

AND

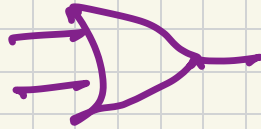

OR

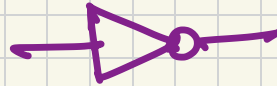

NOT



(Buffer)



NAND



NOR



XOR



Equivalence

Extension to multiple inputs

A gate can be extended to multiple inputs if the binary operation that it represents is commutative and associative.

NAND and NOR are commutative but not associative.

$$(x \downarrow y) \downarrow z = ((x+y)' + z)'$$

$$= ((x+y)')' \cdot z'$$

$$= (x+y) \cdot z' = xz' + yz'$$

$$x \downarrow (y \downarrow z) = (x + (y+z)')'$$

$$= x' \cdot (y+z)$$



$$= x'y + x'z$$

Therefore, we define multiple NOR gate as a complemented OR gate.

$$x \downarrow y \downarrow z = (x + y + z)'$$


Similarly we define multiple NAND gate as a complemented AND gate.

$$x \uparrow y \uparrow z = (xyz)'$$

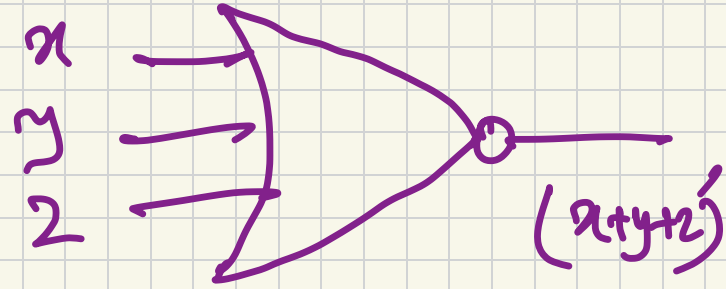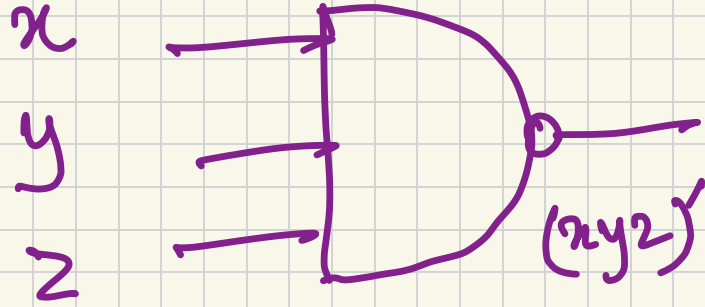

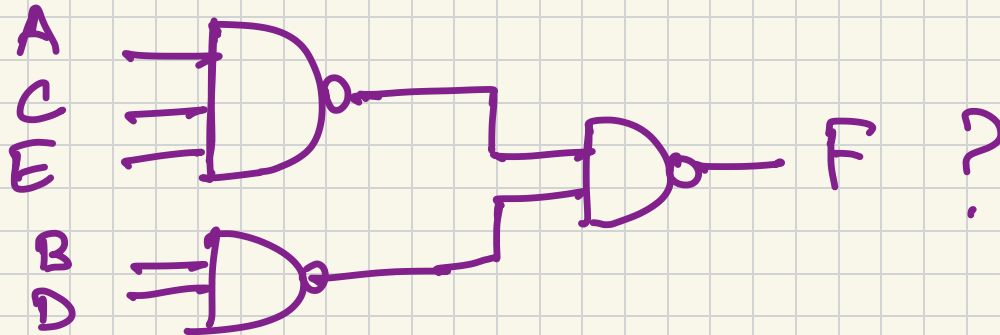Exercise

What is the Boolean function computed by this circuit?




$ACE + BD$

What about XOR?

... XNOR?

Commutative
and
associative

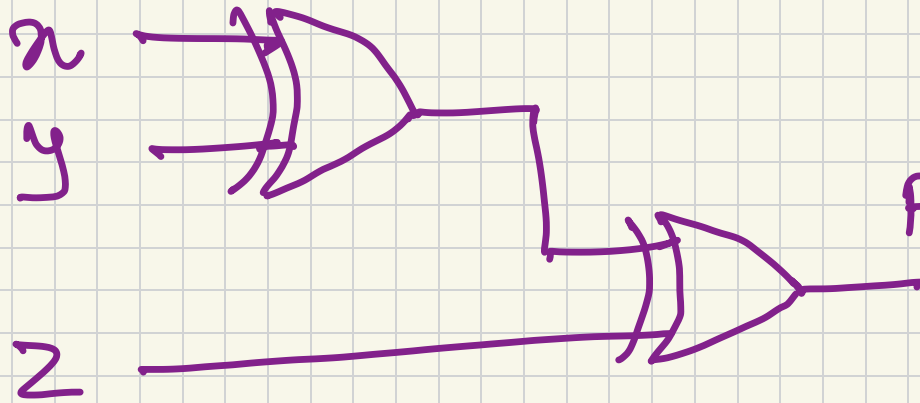

$$F = (x \oplus y) \oplus z$$

Exclusive-OR is an odd function (equals 1 if the input variables have an odd number of 1's).

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Positive and Negative Logic


Hardware digital gates are defined in terms of signal values - H and L.

Two signal values \rightarrow two logic values

1 \rightarrow H	0 \rightarrow H
0 \rightarrow L	1 \rightarrow L

positive logic system negative logic system

Consider the electronic gate

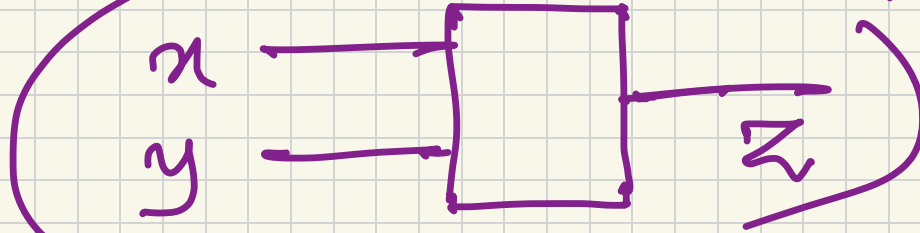


The "physical behaviour" of this gate is specified as

	x	y	z
	L	L	L
	L	H	L
	H	L	L
	H	H	H

If you assume a positive logic system
then we get the following (assignment)
behaviours


x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

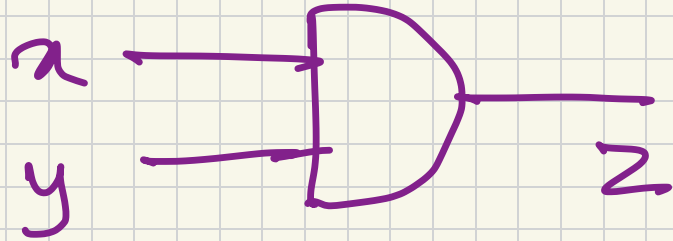

AND gate

If, however, we assume a negative logic system (assignment) then we get the following behaviour.

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0

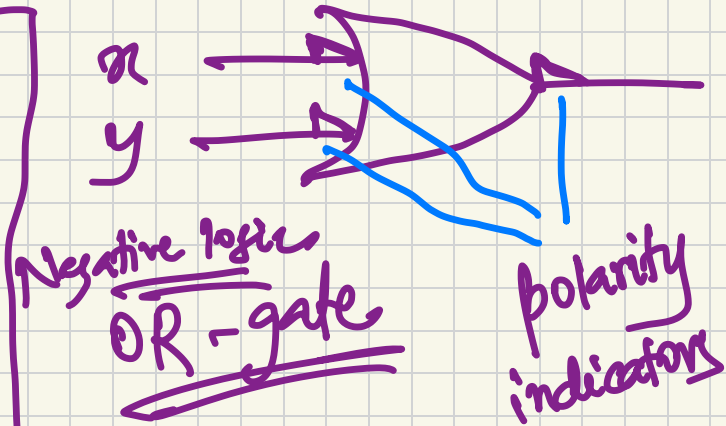

Exercise

Implement the Boolean function

$$F = xz + x'z' + x'y$$

with

i) NAND and NOT (inverter) gates

ii) NOR and NOT (inverter) gates

To be discussed in the next class

Integrated Circuits

called a chip || An IC is fabricated on a die of a silicon semiconductor crystal

on
a microchip

Digital ICs are categorized in terms of complexity of their circuits | the number of logic gates in a single package

Small-scale integration circuits

(SSI)

~ 10 gates in a
single package

Medium | MSI

(~ 10 - 1000 gates)

Large | LSI

(several thousand gates)

Very large | VLSI

(millions of gates)

Ultra large | ULSI

(— " —)

Digital ICs are also classified
by the specific circuit technology
to which they belong.

digital logic family

Some of the popular
ones include

Standard		TTL
high speed		ECL
high component density		MOS
low power		CMOS

Transistor-transistor logic
Emitter-coupled logic
Metal-oxide semiconductor
Complementary " ←

CMOS is used in many handheld portable devices.

Exercise Please read sect. 2.9 from the book.