 


ACOL 215

(Nov. 3)

One way to eliminate the undesirable "forbidden" condition is to ensure that S, R are never 1 at the same time.


# D (Transparent) latch




"Transparent" because D is visible at the output.

En	D	Q
0	X	No change
1	0	$Q = 0$
1	1	$Q = 1$

# Edge-triggered D flip-flop

 

 positive edges (0 to 1)  
negative edges (1 to 0)



When  $CLK = 0$ ,  $Q$  equals  $Y$ .  
(follower is enabled)  
(leader is disabled)

When the clock pulse changes to logic-1 level, leader is enabled, and follower is disabled.

↳ any change in  $D$  does not affect the output.

When the clk now goes from 1 to 0, leader is disabled, and the value of  $\gamma$  is transferred to  $Q$ .

↳ negative edge triggered D flip-flop  
Exercise Construct ~ positive edge triggered D flip flop.