

ACOL 215

(06 Oct.)

## Binary Addition / Subtraction

Addition of two binary digits

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10 \quad \left. \vphantom{1 + 1 = 10} \right\} \text{ produces a carry}$$


A combinational circuit that performs the addition of two bits is called a half-adder.

And one that performs addition of three bits (two bits and a previous carry) is called a full-adder.

$x$	$y$	$S$	$C$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = x'y + xy' \quad (x \oplus y)$$

$$C = xy$$

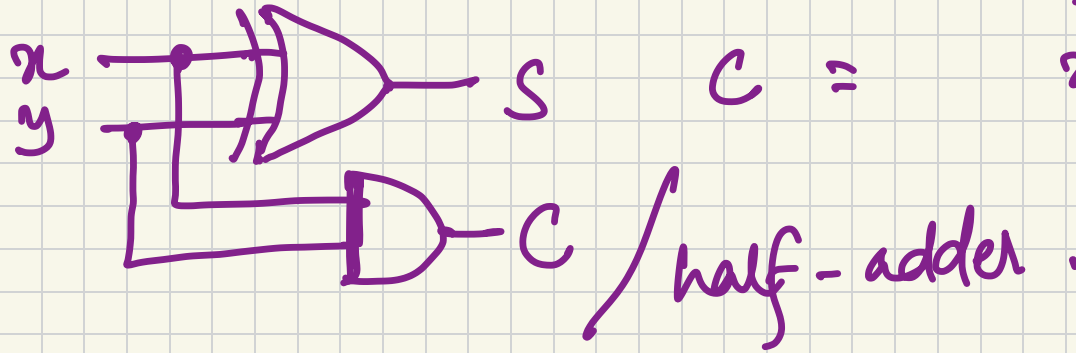

What about a full-adder?  
(carry)

$x$	$y$	$z$	$c$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

		$yz$			
		00	01	11	10
$x$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
		1	1	1	1

$(x \oplus y) \oplus z$

		$yz$			
		00	01	11	10
$x$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$
			1	1	1

$$S = (x \oplus y) \oplus z$$


$$C = xy + xz + yz$$

$$= xy + z(x + y)$$


$$= xy + z((x \oplus y) + xy)$$

$$= \underbrace{xy + zxy} + z(x \oplus y)$$

$$= xy + z(x \oplus y)$$

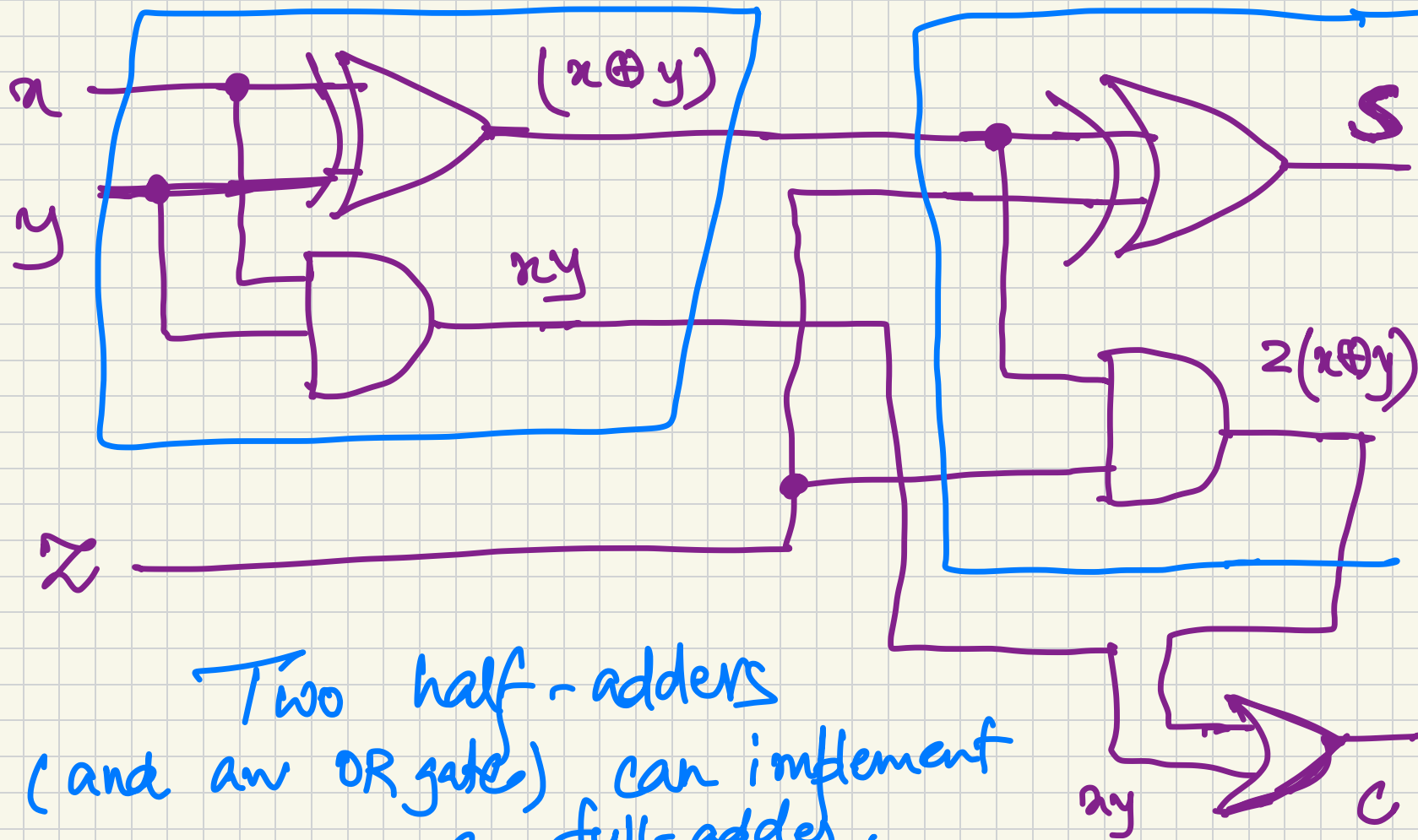


# Binary Adder

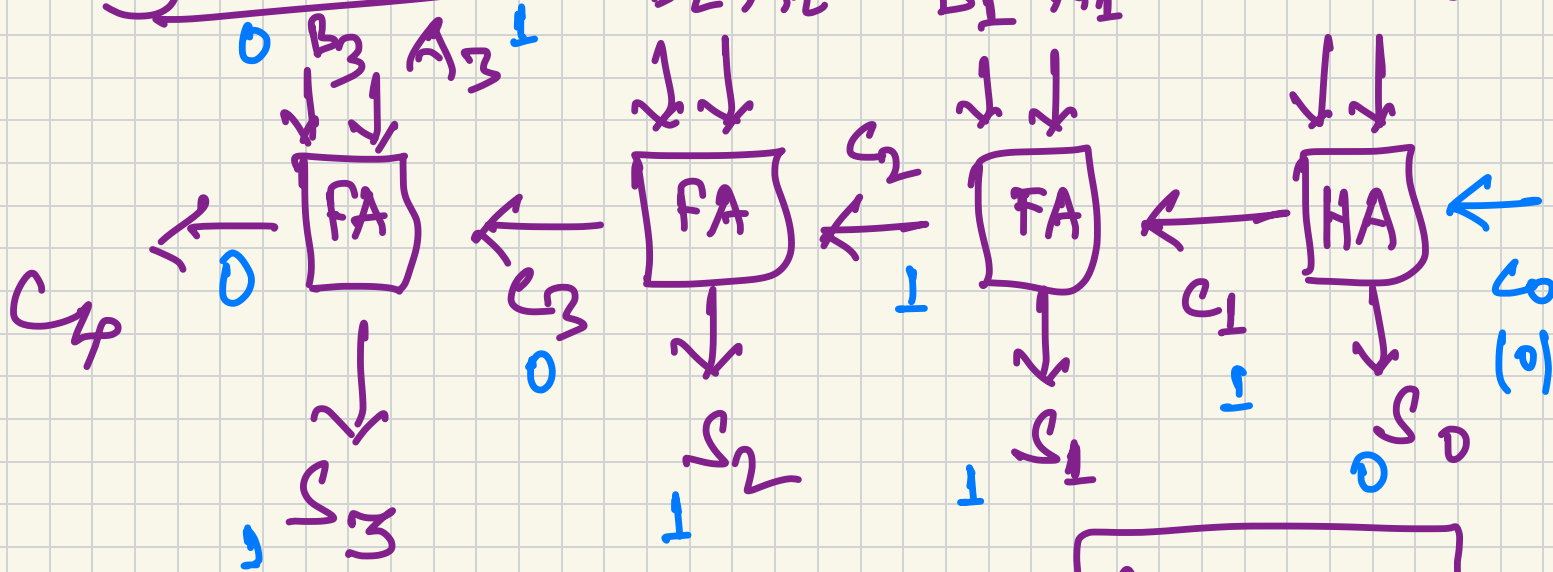

$A = 1011$   
 $B = 0011$

1110

# Carry Propagation

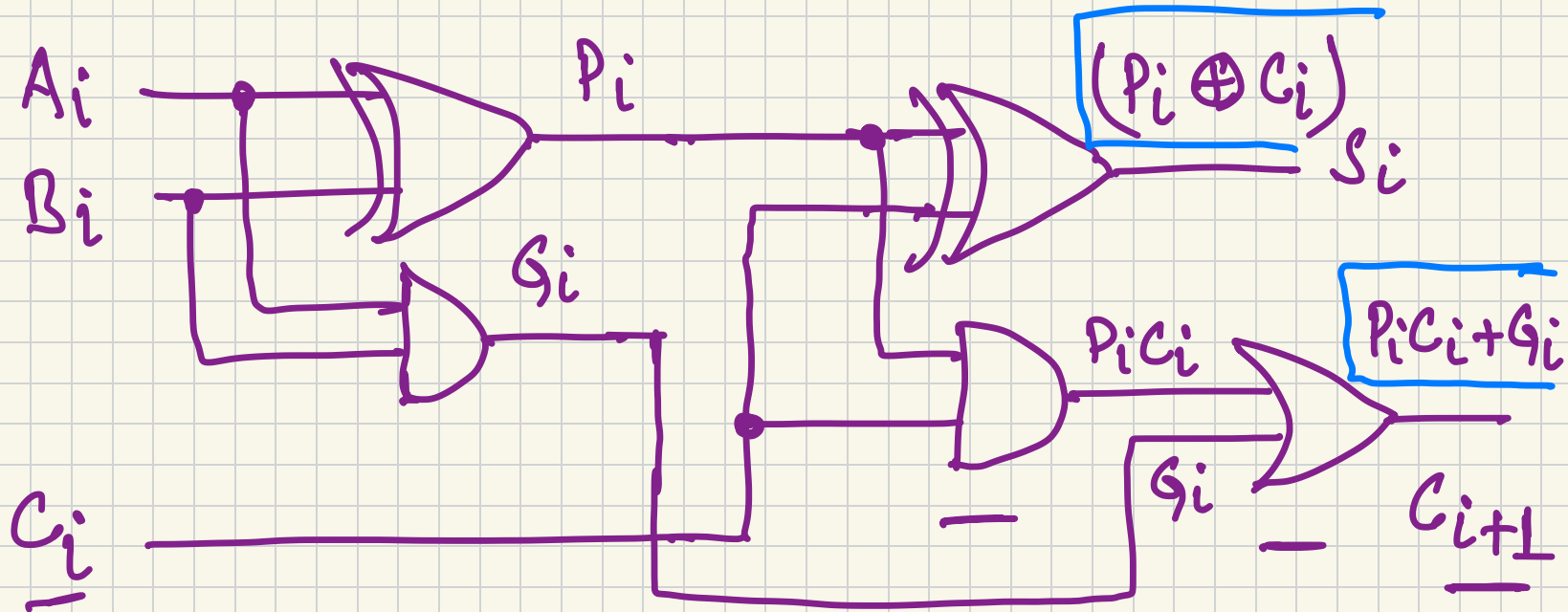

defined two new binary variables

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

→ carry propagate

→ carry generated



$$C_0 = \text{input carry}$$

$$C_1 = P_0 C_0 + G_0$$

$$C_2 = P_1 C_1 + G_1$$

$$= P_1 (P_0 C_0 + G_0) + G_1$$


$$= P_1 P_0 C_0 + P_1 G_0 + G_1$$

$$C_3 = P_2 C_2 + G_2$$

$$= P_2 (P_1 P_0 C_0 + P_1 G_0 + G_1) + G_2$$


$$= P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

# Carry lookahead generator

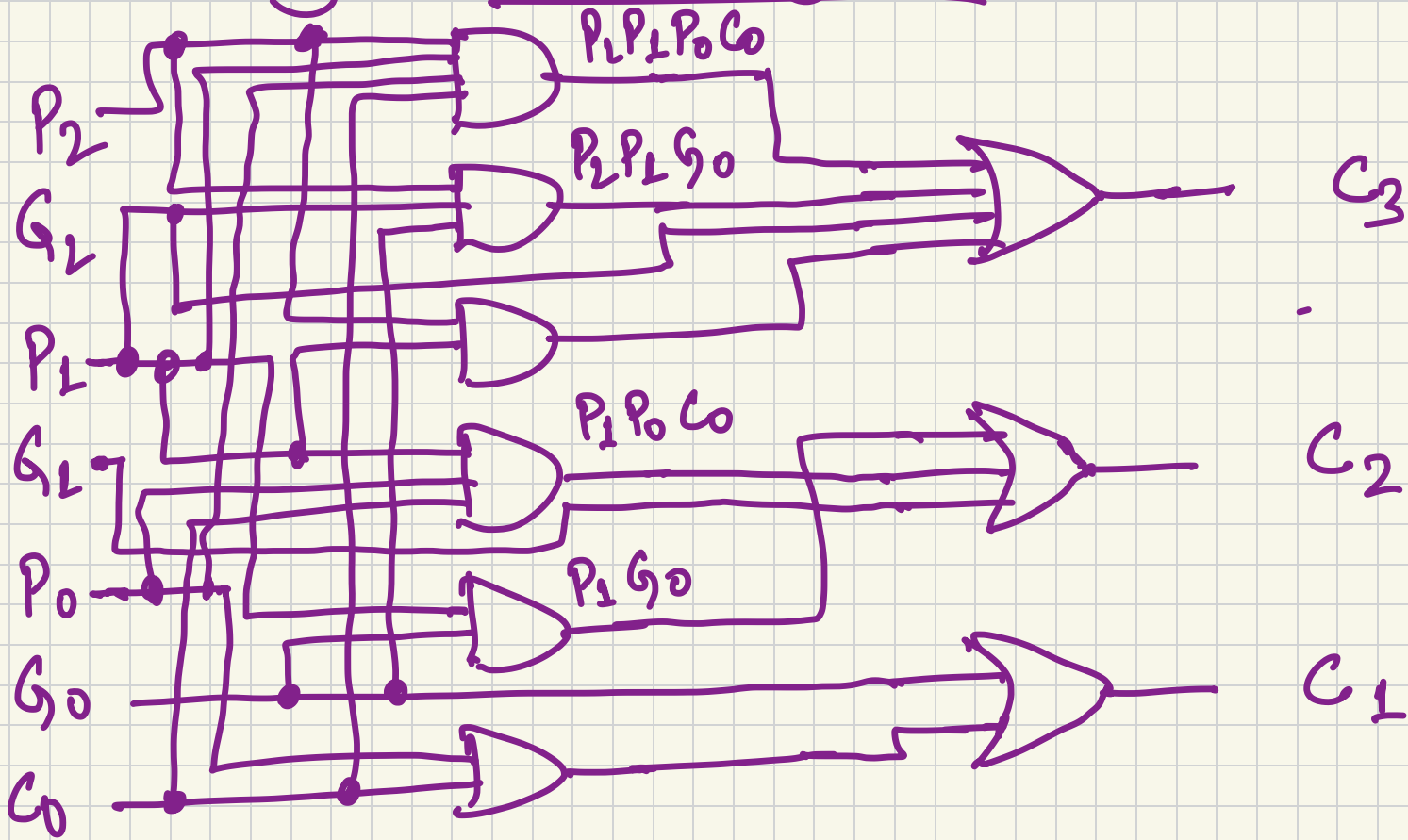

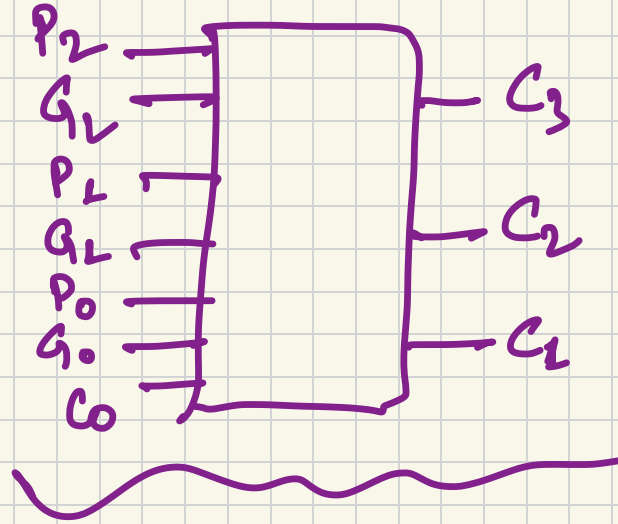
# 4-bit adder

$$P_i = A_i \oplus B_i$$
$$G_i = A_i B_i$$



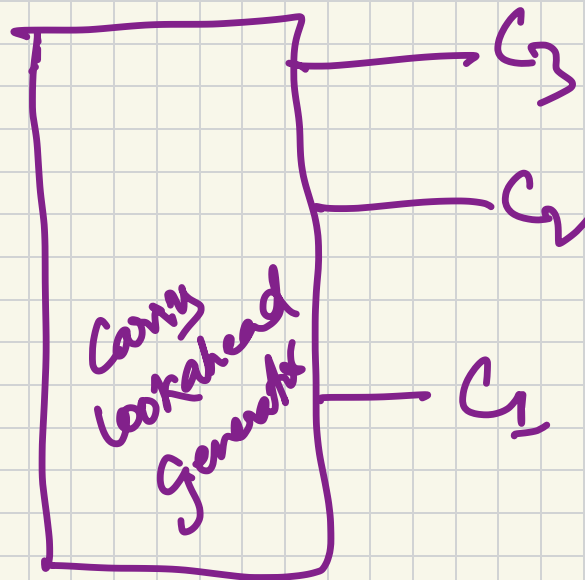$A_3$   
 $B_3$   
 $A_2$   
 $B_2$   
 $A_1$   
 $B_1$   
 $A_0$   
 $B_0$   
 $C_0$



Exercise

Draw a 4-bit binary adder with a carry lookahead generator block.

