


ACOL 215

(Oct. 29)
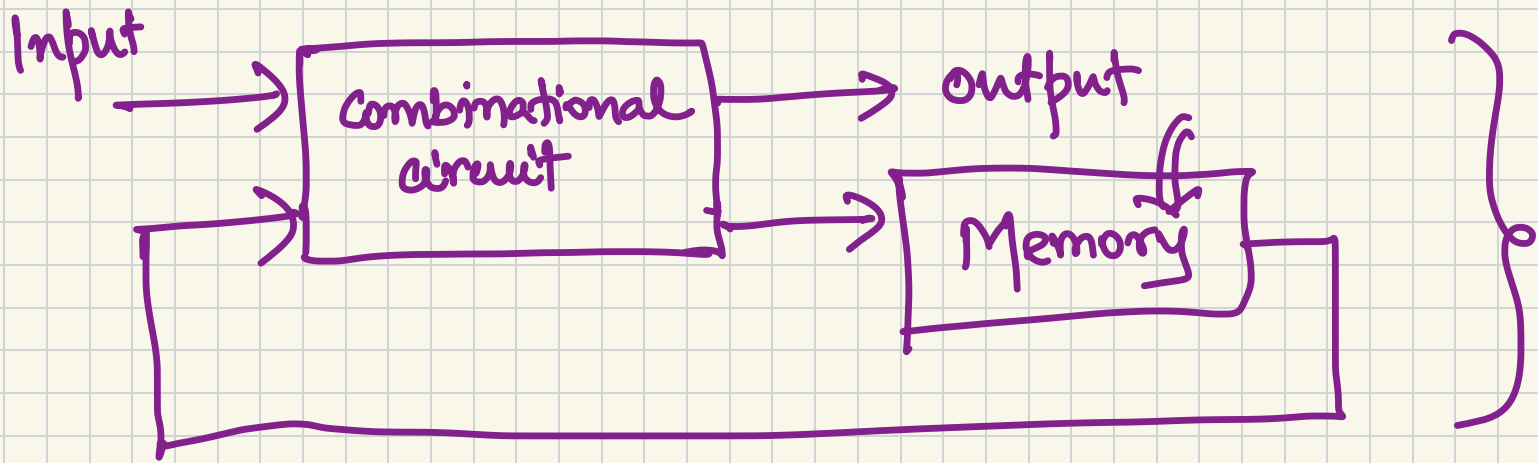
## Synchronous Sequential Logic

Digital electronic devices have components that can store information.

In contrast, the circuits that we have seen so far have been combinational  
↳ outputs depend only (and immediately) on the inputs.



Sequential circuit (Block diagrams)

Synchronous

it employs signals that affect the storage element at only discrete instants of time

Asynchronous

any time

We will restrict ourselves to  
Synchronous sequential circuits.

↳ How is this synchronization  
achieved?


→ through clock signal  
(clk)

clocked sequential  
circuits



periodic sequence  
of clock pulses.

 The storage element used in clocked sequential circuits are called flip-flops.



Note that the speed at which the combinational circuit operates is critical.

If the clock pulses arrive at regular intervals, the combinational circuit must respond to a change in the state of the flip-flop in time (to be updated before the next pulse arrives)


Therefore, propagation delay plays an important role in determining the interval between clock pulses.

Storage elements : Latches

are the basic  
circuit from which flip-flops  
are constructed.

SR Latch  
→

 circuit with two cross-coupled  
NOR gates  
( or two cross-coupled  
NAND gates )



SR Latch  
has two useful  
states

$$Q = 1 ; Q' = 0$$

set state

$$Q = 0 ; Q' = 1$$

reset state

A	B
0	0
0	1
1	0
1	1

A NOR B

1
0
0
0

What happens when  $S = 1, R = 1$  ?

$$Q = 0 ; Q' = 0$$

↳ after this when the inputs are removed

$$(S = 0, R = 0)$$

→

$$Q = 0 ; Q' = 1$$

→

$$Q = 1 ; Q' = 0$$

$$S = 1 ; R = 0$$

inputs are removed ( $S = 0 ; R = 0$ )

$$\boxed{Q = 1 ; Q' = 0} \rightarrow \text{remains in memory}$$

$$S = 0 ; R = 1$$

$$Q = 0 ; Q' = 1$$

when the inputs are removed now  
( $S = 0 , R = 0$ )

$$\boxed{\cancel{Q} = 0 ; Q' = 1} \rightarrow \text{remains in memory}$$




What happens when  $S=1$ ,  $R=1$ ?

$Q=0$  ;  $Q'=0$   
{ after this when the inputs are removed  
( $S=0, R=0$ )  $\rightarrow$   $Q=0$  ;  $Q'=1$  }  
 $\rightarrow$   $Q=1$  ;  $Q'=0$  }


Therefore, setting both  $S$  and  $R$   
to 1 is forbidden.

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S=1, R=0$ )
0	1	0	1	
0	0	0	1	(after $S=0, R=1$ )
1	1	0	0	(forbidden)

# SR latch with NAND gates

 

Exercise  
Verify

 

S	R
1	0
1	1
1	1

0	1
1	1
1	1

0	0
0	0

Q	Q'
0	1
0	1


(after  $S=1, R=0$ )

1	0
1	0

(after  $S=0, R=1$ )

1 1 (forbidden)

# SR latch with control input

 

When  $En = 0$ , there is no change in  $Q$  and  $Q'$

When  $En = 1$ , we are effectively having  $S'$  and  $R'$  after the first-level NAND gates

$En$	$S$	$R$
1	0	0
1	0	1
1	1	0
1	1	1

No change

$Q = 0$ ,  $Q' = 1$

$Q = 1$ ,  $Q' = 0$

forbidden