

ACOL 215

(Nov. 17th)

Clocked Sequential Circuits


- Registers
- Counters

Registers

- group of flip flops connected by a common clock
- each flip-flop can store one bit

load \rightarrow

4-bit
data
storage
register

 

reset input
goes to the
active-low
R input of
the flip
flops
 \downarrow
when reset is
0 all flip
flops are
reset asynchronously

The transfer of new inputs into a register is called "loading" the register.


→ if all bits are loaded simultaneously, then it is said that the loading is done in parallel.

If the content of a register must be left unchanged, we must either

- maintain the inputs
- prevent the clock pulse from reaching the circuit.


We will gate the data path instead

 this can be done by clock gating → not a good idea




Shift Registers

 A register capable of shifting the binary information held in each cell to its neighboring cell.




Serial Transfer

 

	A	B
Beginning	1011	0011
After 1st pulse	1101	1001
2nd pulse	1110	1100
3rd pulse	0111	0110
4th pulse	1011	1011

Serial Addition

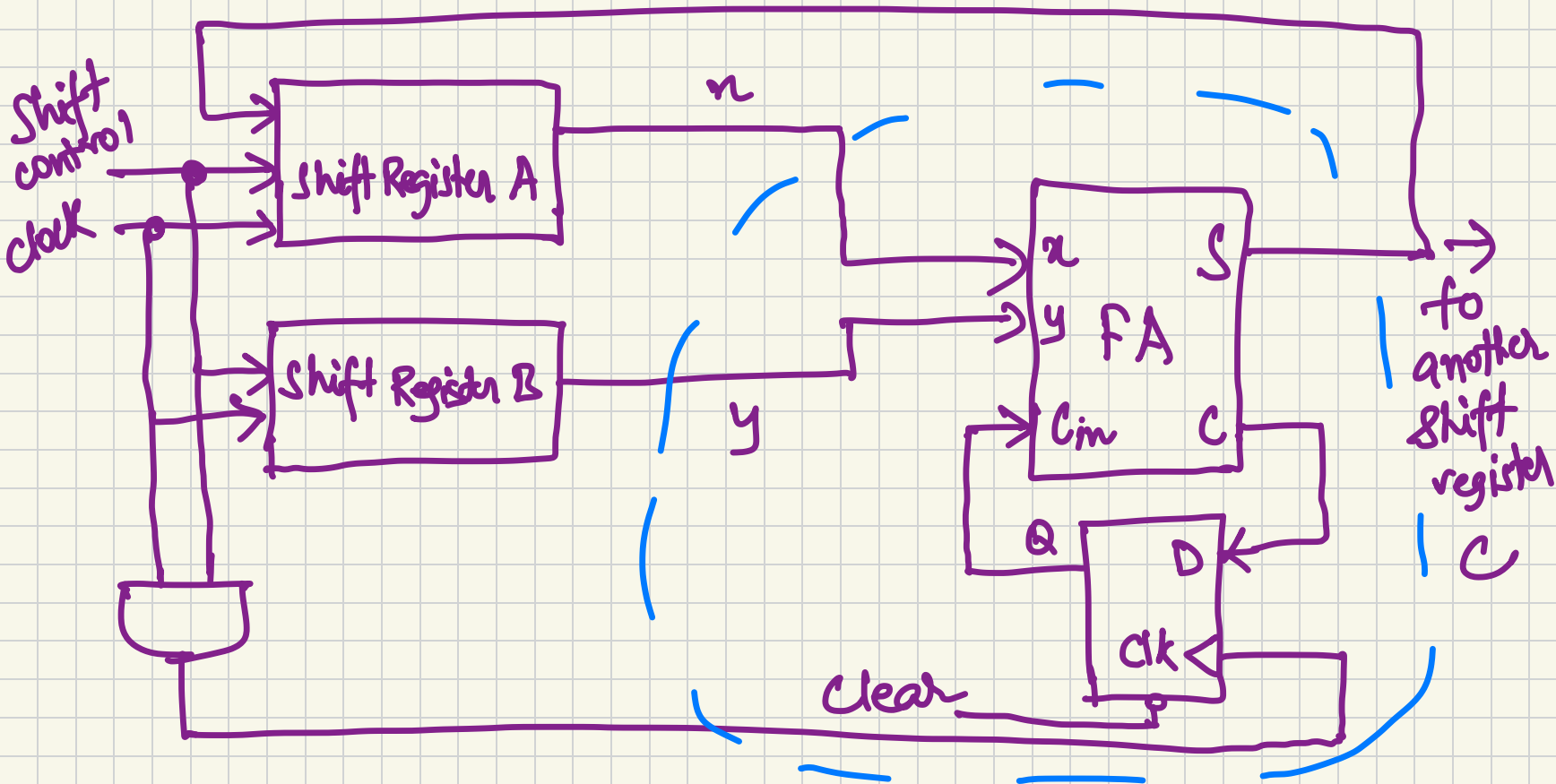

Serial Adder State Table

Present State	Inputs		Next State	Output	Flip-flop inputs	
<u>Q</u>	<u>x</u>	<u>y</u>	<u>Q</u>	<u>S</u>	<u>J_Q</u>	<u>K_Q</u>
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	1	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	0	1	X	0

J	K
0	0
0	1
1	0
1	1

$Q(t+1)$
$Q(t)$
0
1
$Q'(t)$

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

		xy			
		00	01	11	10
Q	0	0	0	1	0
	1	X	X	X	X


		xy			
		00	01	11	10
Q	0	0	1	0	1
	1	1	0	1	0

$$\underline{S = Q \oplus x \oplus y}$$

$$\underline{J_Q = xy}$$

$$K_Q = x'y' \quad (x+y)'$$

		xy			
		00	01	11	10
Q	0	X	X	X	X
	1	1	0	0	0

 

Exercise \rightarrow Implement using D flip flop.