


Quiz 3

(Solutions)

 1. Clearly, the inputs are the two lines
- call them A_1 and A_2 . There is also
an enable input - let us call it E .

The outputs clearly are $A_1'A_2'E$,
 $A_1'A_2\bar{E}$, $A_1A_2'E$, and A_1A_2E .

The logic diagram can be
drawn using NOR and inverters
as follows.



2.


D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z	v
0	0	0	0	0	0	0	0	X	X	X	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1

The row enclosed in a blue rectangle is the one that corresponds to D_3 and D_5 being 1, and everything else being 0.



The corresponding output, as clearly seen in the table is

x	y	z	v
1	0	1	1


 
3. Here is the D (transparent) latch using four NAND gates (and an inverter).




  Let us try to modify this step-by-step to get the desired form.



  These are NOR gates now \rightarrow in invert-AND representation.



 

We can verify that this circuit behaves as per the following function table.

En	D	$Q(t+1)$
0	X	$Q(t)$
1	0	0
1	1	1

4. Recall, from the mid-term paper, that the truth table of a full subtractor is as follows.

x	y	B_{in}	B_{out}	D	B_{out}	D
0	0	0	0	0	B_{in}	B_{in}
0	0	1	1	1		
0	1	0	1	1	1	B_{in}'
0	1	1	1	0		
1	0	0	0	1	0	B_{in}'
1	0	1	0	0		
1	1	0	0	0	B_{in}	B_{in}
1	1	1	1	1		

