

---

Name:

Entry No.:

---

*Please show all the steps in your solution clearly. Writing the final answer directly would not fetch any marks.*

---

1. [1 mark] Convert decimal (+49) and (+29) to binary, using the signed-2's-complement representation and enough digits to accommodate the numbers. Then perform the binary equivalent of  $(+29) + (-49)$ , and  $(-29) + (-49)$ . Convert the answers back to decimal and verify that they are correct.
2. [1 mark] Convert each of the following expressions into sum of products and product of sums.
  - (a)  $(w + xy')(x + y'z)$
  - (b)  $xy + (w' + y'z')(z' + x'y')$
3. [1.5 mark] Implement the following Boolean function  $F$ , together with the don't-care conditions  $d$ , using no more than two NOR gates.

$$F(A, B, C, D) = \Sigma(2, 4, 10, 12, 14)$$
$$d(A, B, C, D) = \Sigma(0, 1, 5, 8)$$

4. [1.5 mark] Implement the following Boolean function  $F$ , using the two-level forms *i)* AND-NOR, and *ii)* OR-NAND.

$$F(A, B, C, D) = \Sigma(0, 4, 8, 9, 10, 11, 12, 14)$$