

ACOL215

(Oct. 8th)

Decoders


A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n output lines.

In particular, we look at

n -to- m -line decoders,

where $m \leq 2^n$.

 A binary code of n bits can represent 2^n distinct elements of coded information.




Some decoder are constructed with NAND gates } for efficiency

→ complemented output

Decoders can have one or more enable inputs to control the circuit operation.

A B E

 

↓ circuit operation.

E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Two-to-four line decoder with an enable input constructed with NAND gates

complemented input

NAND
gates

& complement
enable input

Outputs are
enabled when
 $E = 0$

(active-low
enabled)

A decoder with enable
input can function as a demultiplexer

→ a circuit that receives information
from a single line and directs it to
one of 2^n possible output lines.

E can be thought of as data input line and A, B as selection input lines.


→ For different selection inputs, E is directed to different outputs.

When AB is 10, E is directed to D_2 .

AB is 11, E is directed to D_3 .

A decoder with an enable input is also called a decoder demultiplexer.

 Decoders with enable inputs can be connected to form a larger decoder circuit.



Implement a full-adder with a decoder.

x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

C	S
0	0
0	1
0	1
1	0
0	1
1	0
1	0
1	1

$$S(x, y, z)$$

$$= \sum (1, 2, 4)$$


$$C(x, y, z)$$

$$= \sum (3, 5, 6, 7)$$

x

y

z

 

Encoder

inverse operation of a decoder

2^n (or fewer) input lines

→ n output lines.

Example: octal to binary encoder

$$\begin{aligned}
 x &= D_4 + D_5 + D_6 + D_7 \\
 y &= D_2 + D_3 + D_6 + D_7 \\
 z &= D_1 + D_3 + D_5 + D_7
 \end{aligned}$$

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

If D_5 and D_6 are 1 at the same time the output is 111 (which is absurd).

→ Fixed by assigning higher priority to higher index input.

If all inputs are 0, then output is 000 which is the code when $D_0 = 1$.

→ Fixed with a valid bit indicator.

D_0 D_1 D_2 D_3

0 0 0 0

1 0 0 0

X 1 0 0

~~X~~ ~~0~~ 1 0

~~X~~ ~~0~~ ~~0~~ 1

0
0
0

0
0
1

0
1
0

1
1
1

X
1

X
0

X
0

1

x y v

X X 0

0 0 1

0 1 1

1 0 1

1 1 1

00 01 11 10

00 X 1 1 0

10 0 1 1 0

11 1 1 1 0

1 1 1 0

$D_2 D_3$

$D_0 D_1$

	00	01	11	10
00	X	1	1	1
01		1	1	1
11		1	1	1
10		1	1	1


D_3


$$x = D_2 + D_3$$

y?


$$V = D_0 + D_1 + D_2 + D_3$$

$$D_1 \cdot D_2' + D_3$$

 

 

Multiplexers

 

$S = 0$	I_0
$S = 1$	I_1