

Quiz 1

(Solutions)

Q1. $+49$ in binary : 00110001
 $+29$ in binary : 00011101

Signed-2's-complement representation of
 -29 can be obtained by first taking
Signed-1's complement of -9 (which can
be obtained by flipping the bits of $+29$)
and then adding 1.

-29 in signed-2's complement is

$$\begin{array}{r} 11100010 \\ + \quad 1 \\ \hline 11100011 \end{array}$$

Similarly, -49 is signed -2's complement

$$\begin{array}{r} 11001110 \\ + \quad 1 \\ \hline 11001111 \end{array}$$

Thus,

$$\begin{array}{r} +29 \\ +(-49) \end{array} \text{ is } \begin{array}{r} 00011101 \\ + 11001111 \\ \hline 11101100 \end{array}$$

How do we know this is correct (-20) ?

2's complement of this is

$$\begin{array}{r} 00010011 \\ + \quad 1 \\ \hline 00010100 \end{array}$$

which evaluates to 20.

Similarly,

$$\begin{array}{r} (-29) \\ +(-49) \end{array} \text{ is } \begin{array}{r} 11100011 \\ + 11001111 \\ \hline 10110010 \end{array}$$

We know this is -78 because 2's complement of this answer gives

$$\begin{array}{r} 01001101 \\ + \quad 1 \\ \hline 01001110 \end{array}$$

which is 78.

$$Q2. \quad a) \quad (w+xy')(x+y'z)$$

$$= wx + wy'z + xy' + xy'z$$

$$= wx + wy'z + xy'(1+z)$$

$$= wx + wy'z + xy' \quad \left\{ \text{sum of products form} \right.$$

Let us use K-map

to get a sum of products form for the complement.

Complement of the function is

$$w'n' + w'y + x'y + wx'z'$$

Taking its complement again, we get product of sums expression of the original function.

K-map for the function $f(w, x, y, z)$:

			y			
			00	01	11	10
w	00	0	0	0	0	0
	01	1	1	0	0	
	11	1	1	1	1	
	10	0	1	0	0	
			z			

$$\begin{aligned}
 & (w'x' + w'y + x'y + wx'z')' \\
 &= (w'x')' \cdot (w'y)' \cdot (x'y)' \cdot (wx'z')' \\
 &= (w+x) \cdot (w+y') \cdot (x+y') \cdot (w'+x+z)
 \end{aligned}$$


Ans.

Similarly for part (b)

$$\begin{aligned}
 & xy + (w'+y'z')(z'+x'y') \\
 &= xy + w'z' + w'x'y' + y'z' + x'y'z'
 \end{aligned}$$

Sum of products form

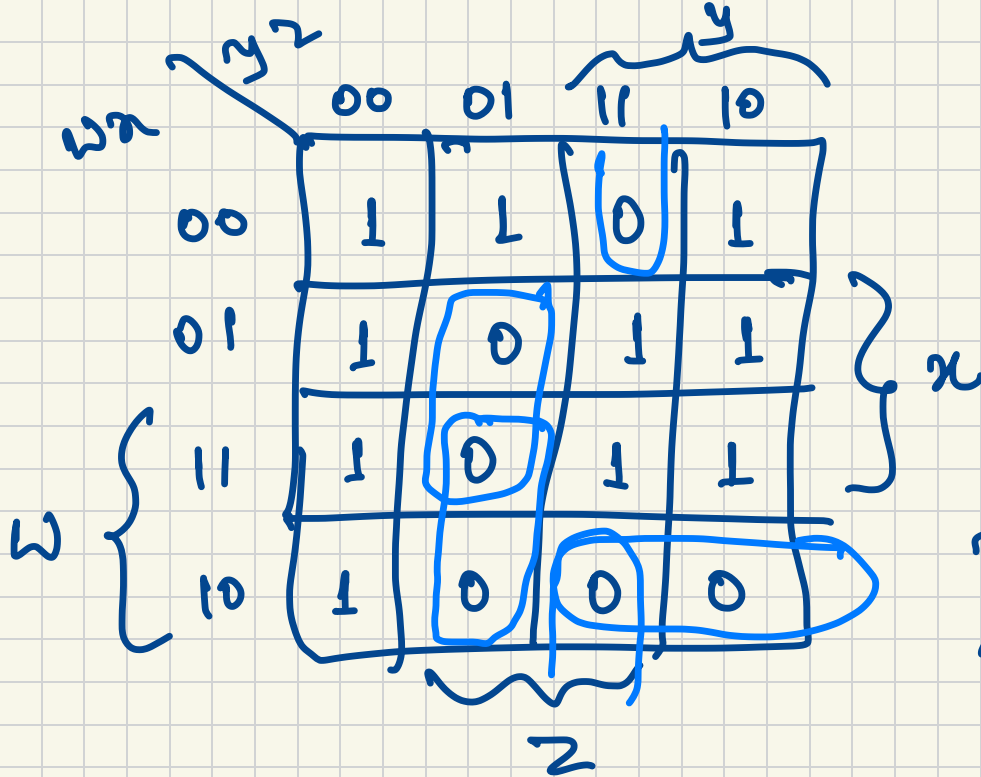We use K-map to get the complement is sum of products form.




Complement of the function is

$$wx'y + wy'z + xy'z + x'yz$$

Taking the complement again, we get the desired form

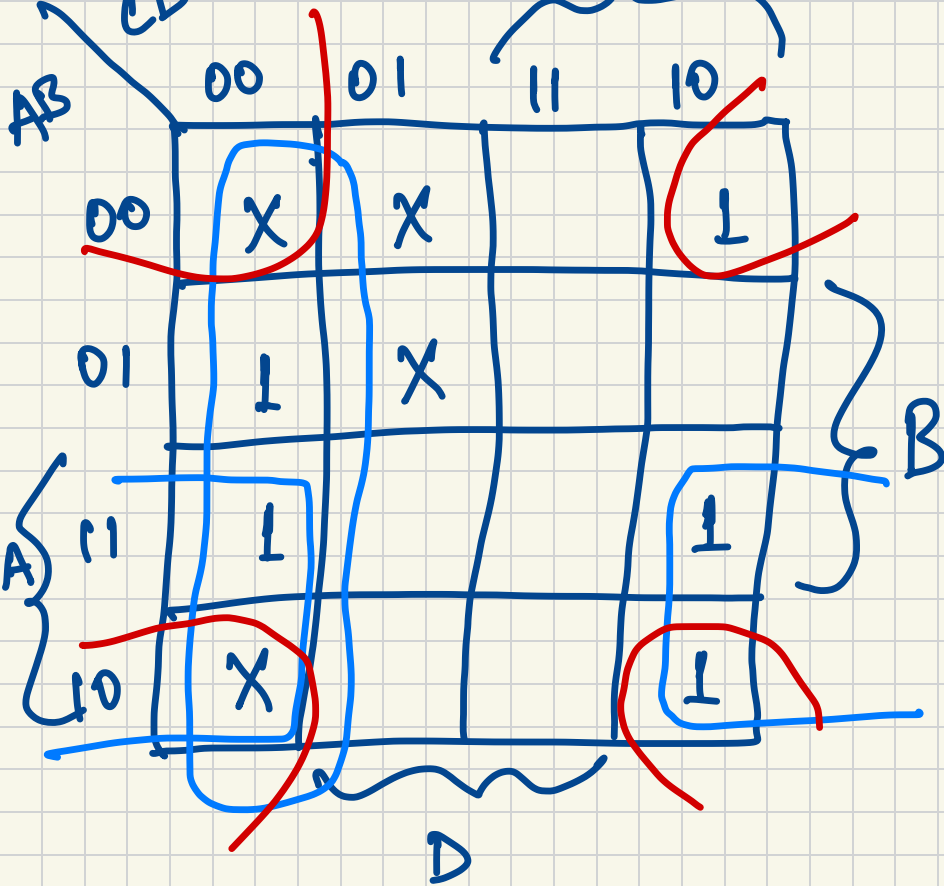
$$\begin{aligned} & (wx'y + wy'z + xy'z + x'yz)' \\ &= (wx'y)' \cdot (wy'z)' \cdot (xy'z)' \cdot (x'yz)' \\ &= (w' + x + y') \cdot (w' + y + z') \cdot (x' + y + z') \cdot (x + y' + z') \end{aligned}$$




$$F = AD' + C'D' + B'D' \\ = D'(A + C' + B')$$

$$= D'(A + C' + B')$$


$$P' = D + A'CB$$

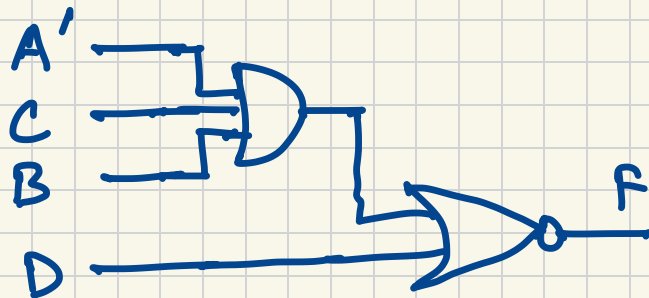

This can also be drawn as

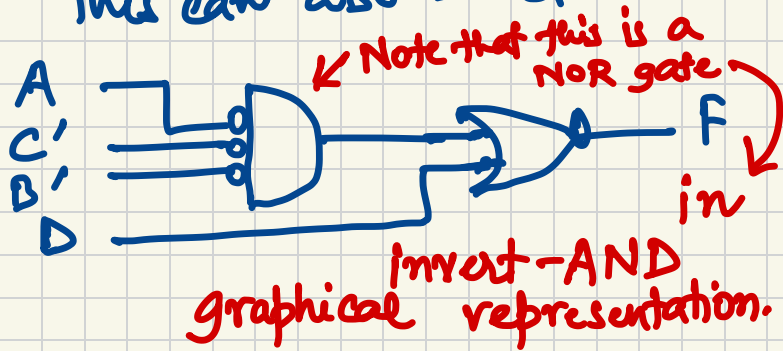

Q4.

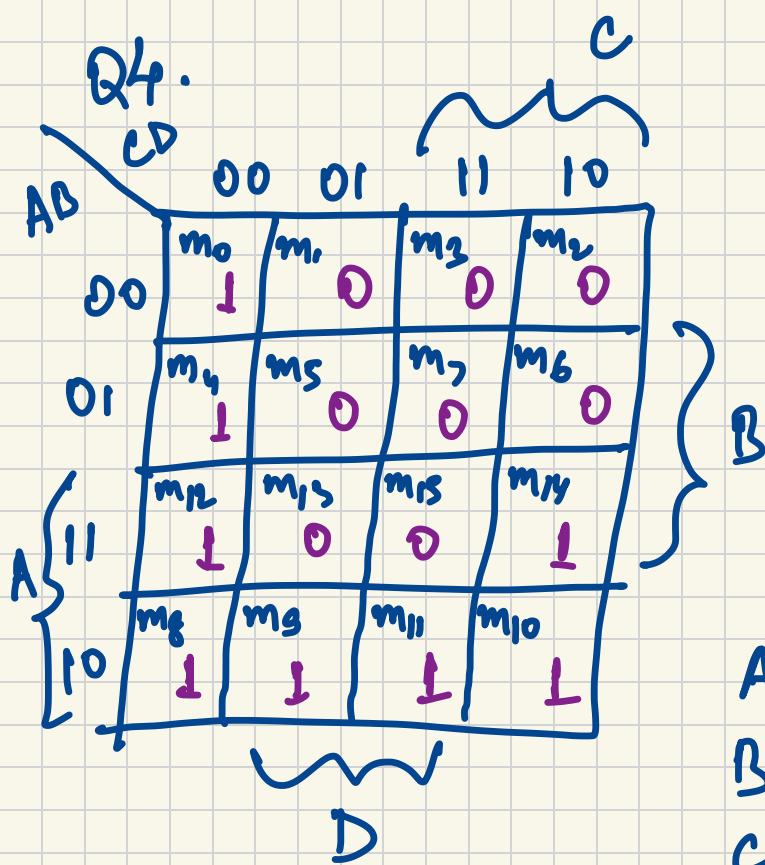


By looking at 1s in the K-map and merging them, we get,

$$f = C'D' + AB' + AD'$$

$$f' = (C + D) \cdot (A' + B) \cdot (A' + D)$$

$$F = ((C + D) \cdot (A' + B) \cdot (A' + D))'$$

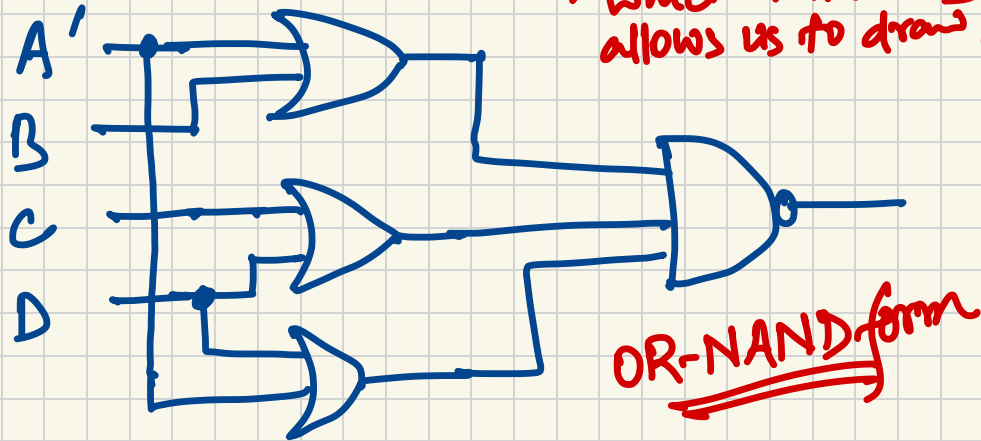OR-AND-Invert form
↓ which immediately allows us to draw!



OR-NAND form


Also, by looking at 0's in the same K-map and merging them, we get

$$F' = (BD + DA' + CA')$$

$$F = (BD + DA' + CA')'$$

AND-OR-Invert form

↓
which immediately allows us
to draw

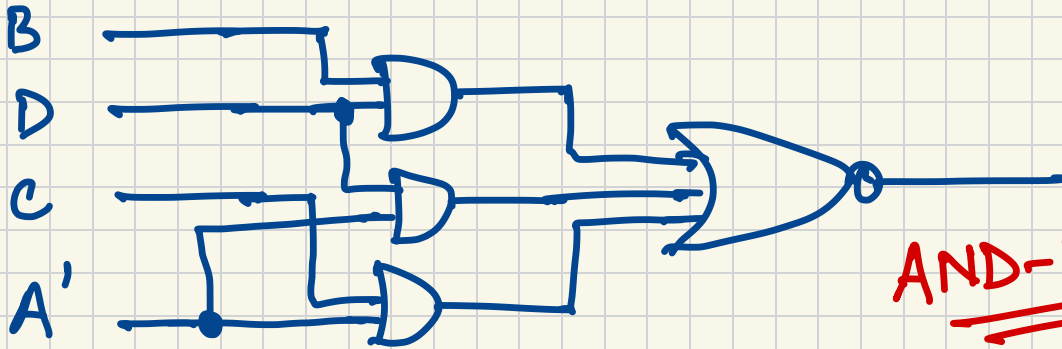

AND-NOR form

Ans.